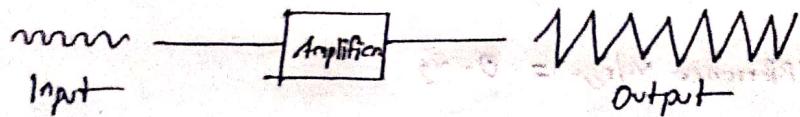


OP-AMP \longrightarrow Operational Amplifier

Introduction to op-amp




Op-amp

• 2 input & 1 output

• 2 power supply

Non-Inverting Input
Inverting Input

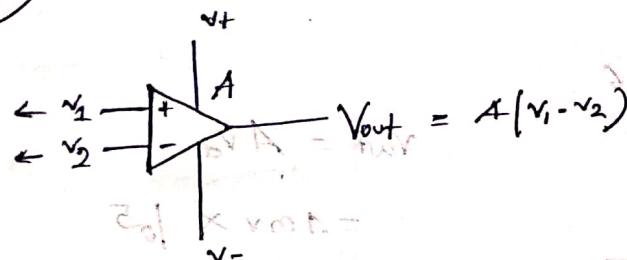


Let's say, v_1 & v_2 are the input signals

& gain of the operational Amplifier A

$$V_{out} = A(v_1 - v_2)$$

#

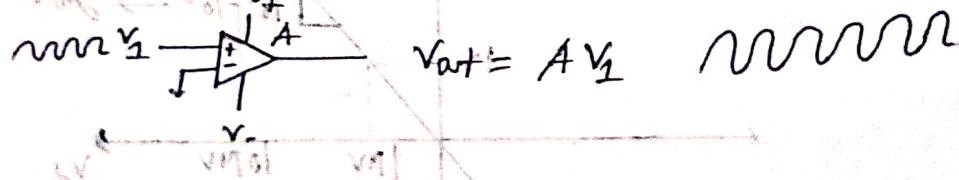

Voltage Difference

$$v_1 - 0$$


$$= v_1$$

OP-AMP Equivalent Circuit

R_i = Input Impedance

R_o = Output " "

$$V_{out} = A(v_d)$$

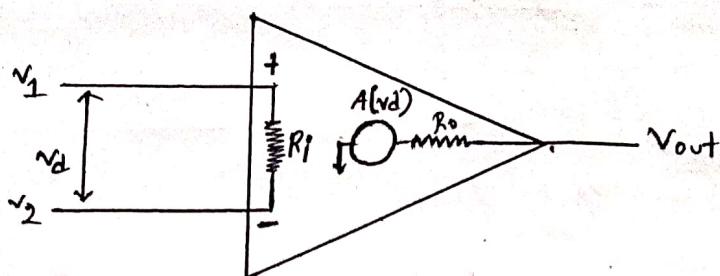

Characteristics of ideal OP-AMP


- $R_i = \infty$
- $R_o = 0$
- Bandwidth = ∞
- gain $A = \infty$
- Slew rate = ∞

• CMRR = Common Mode Rejection Ratio

↳ If $v_1 = v_2$ then $V_{out} = 0$


$$= \frac{A_d}{A_c} = \frac{\text{differential gain}}{\text{Common Mode gain}} = \infty$$

Schmitt Trigger Explained

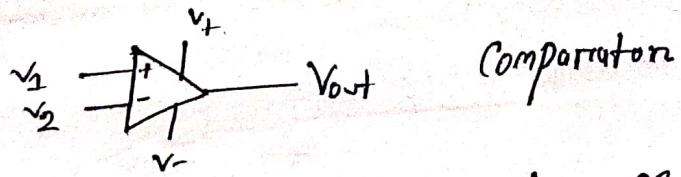

- ⇒ If input signal is Noisy then output will be affected.
- ⇒ This kind of noise problem can be avoided by using

[Schmitt Trigger]

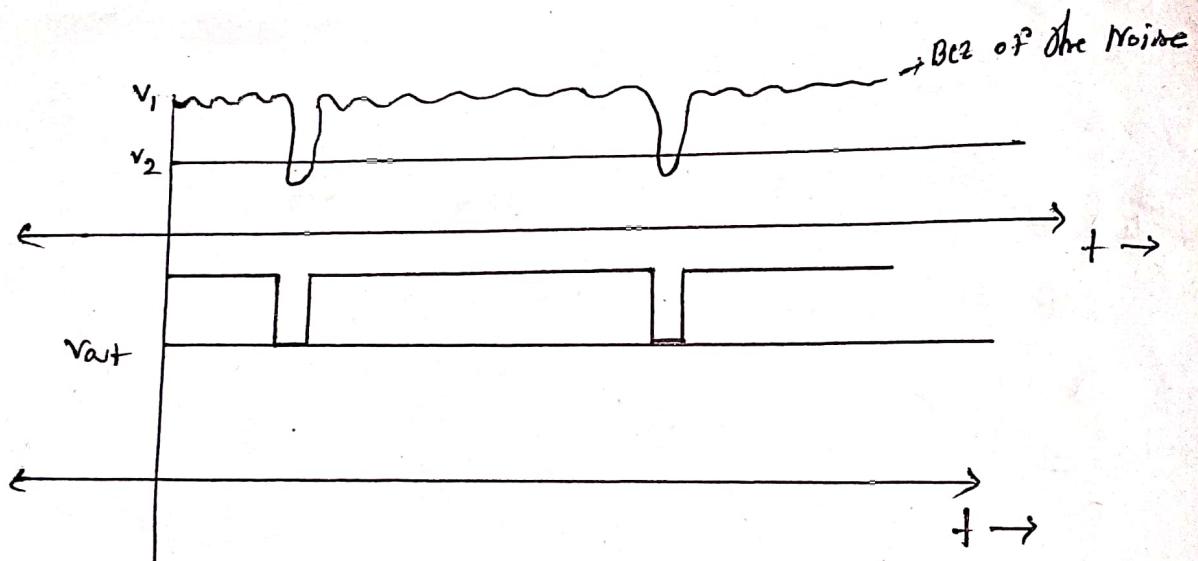

Schmitt Trigger




Schmitt Trigger = Comparator with Hysteresis.

It means that, Schmitt Trigger has 2 Threshold Voltage:

1. Upper Threshold Voltage \rightarrow Low to High

2. Lower " " " \rightarrow High to Low

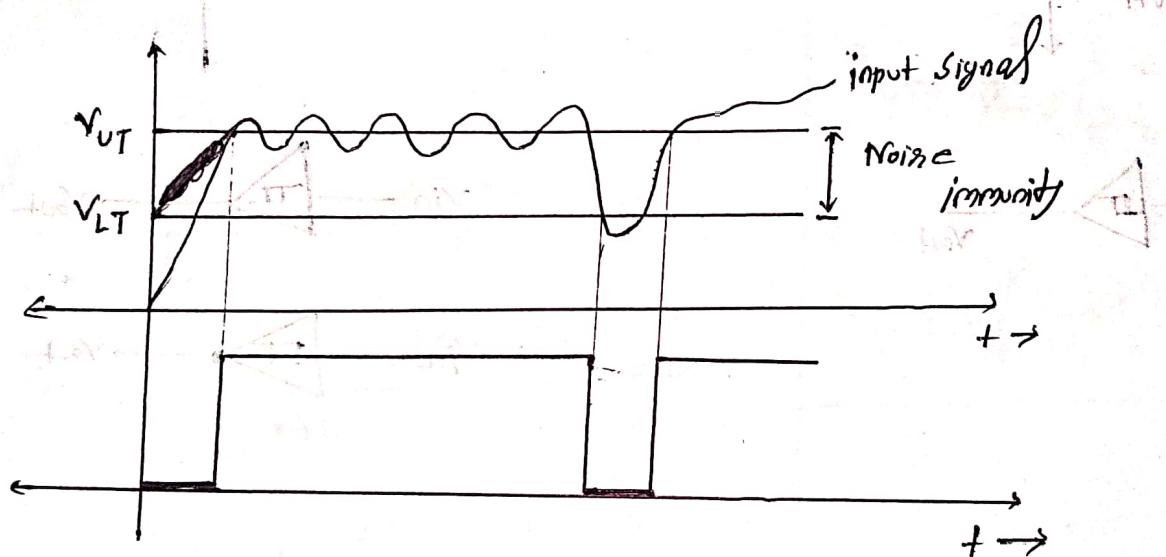

$$\text{# Hysteresis Voltage} = V_{UT} - V_{LT}$$






If input signal less than V_{UT} then output remain Low

As soon as it cross the V_{UT} then output will become High


As soon as input signal goes below V_{LT} then output will become Low

Schmitt Trigger

Inverting Schmitt Trigger

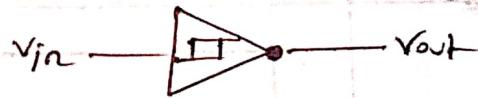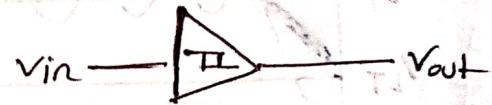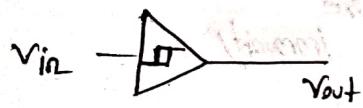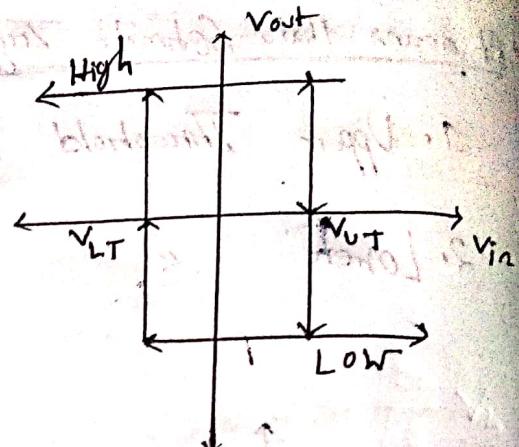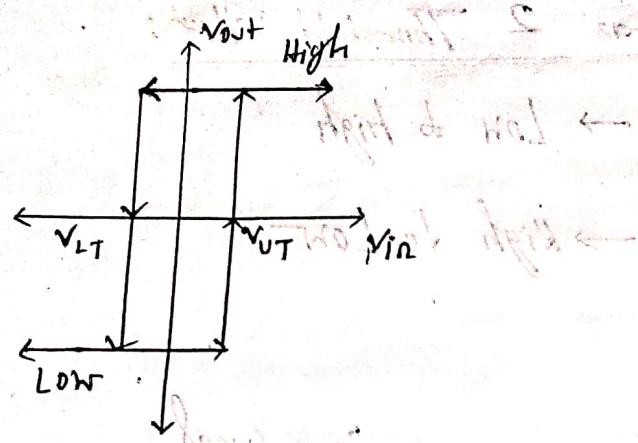

Inverting Schmitt trigger with op-amp

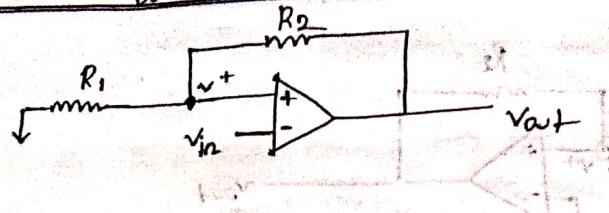

When, $V_{in} > V^+ \Rightarrow V_{out} = V_L$

$V_{in} < V^+ \Rightarrow V_{out} = V_H$

Applying $\frac{V_{CL}}{V^+}$,

$$\frac{V^+ - 0}{R_1} + \frac{V^+ - V_{out}}{R_2} = 0$$

$$H \times \frac{V^+ - V^+}{R_1} + \frac{V^+ - V_{out}}{R_2} = 0$$

$$\Rightarrow \frac{V^+ R_2 + V^+ R_1 - R_1 V_{out}}{R_1 R_2} = 0$$

$$\Rightarrow V^+ R_2 + V^+ R_1 = R_1 V_{out}$$

$$\Rightarrow V^+ (R_1 + R_2) = R_1 V_{out}$$

$$\Rightarrow V^+ = -\frac{R_1}{R_1 + R_2} V_{out}$$

$$V_{UT} = \frac{R_1}{R_1 + R_2} \times V_H$$

$$V_{LT} = \frac{R_1}{R_1 + R_2} \times V_L$$


$$V^+ = V_H \pm \Delta V$$

$$V^+ = V_L \pm \Delta V$$

$$V^+ = V_H \pm \Delta V$$

$$V^+ = V_L \pm \Delta V$$

Non-Inverting Schmitt Trigger

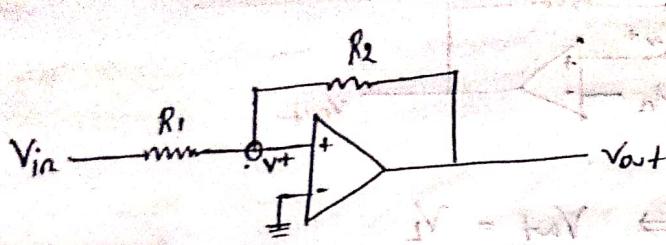

$$V^+ > 0 \Rightarrow V_{out} = V_H$$

$$V^+ < 0 \Rightarrow V_{out} = V_L$$

Applying KCL,

$$\frac{V^+ - V_{in}}{R_1} + \frac{V^+ - V_{out}}{R_2} = 0$$

$$\Rightarrow V^+ \left[\frac{1}{R_1} + \frac{1}{R_2} \right] = V_{in} \frac{1}{R_1} + \frac{V_{out}}{R_2}$$

$$\Rightarrow V^+ \left[\frac{R_2 + R_1}{R_1 R_2} \right] = \frac{V_{in}}{R_1} + \frac{V_{out}}{R_2}$$

$$\Rightarrow V^+ = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_{out}$$

$$\Rightarrow V^+ = \frac{R_2}{R_1 + R_2} V_{in} + \frac{R_1}{R_1 + R_2} V_{out}$$

$$V_H > V_L \Rightarrow V_{out} = V_H$$

$$\star \quad \frac{R_2}{R_1 + R_2} V_{in} > -V_L \cdot \frac{R_1}{R_1 + R_2} \Rightarrow V_{in} > -\frac{R_1}{R_2} \times V_L$$

$$V_{UJ} = -\frac{R_1}{R_2} \times V_L$$

$$V_{LT} = -\frac{R_1}{R_2} \times V_H$$

$$= (V_H + V_L) / 2$$

$$= (V_H - V_L) / 2$$

$$= V_{avg}$$

$$= V_{mid}$$


$$= V_{mean}$$

$$= V_{center}$$

$$\# \text{ Duty Cycle} = \frac{\text{ON time Pulse}}{\text{Total time}} = \frac{T_{on}}{T}$$

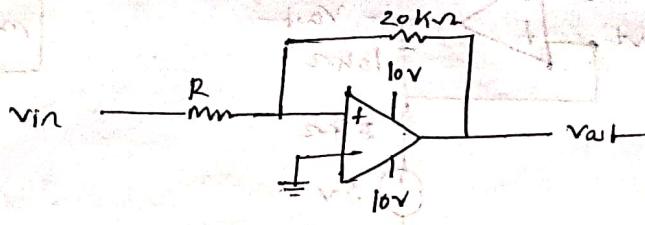Example-2

Find the value of R_1 such that circuit has $1V$ of Hysteresis width



Given

This is Non-inverting Schmitt trigger

Hence

$$R_2 = 20\text{k}\Omega, V_H = 10\text{V}, V_L = -10\text{V}$$

$$\begin{aligned} V_{UT} &= -\frac{R_1}{R_2} V_L \\ &= -\frac{R_1}{R_2} \times -10\text{V} \\ &= 10 \frac{R_1}{R_2} \end{aligned}$$

$$\begin{aligned} V_{LT} &= -\frac{R_1}{R_2} V_H \\ &= -\frac{R_1}{R_2} \times 10\text{V} \\ &= -10 \frac{R_1}{R_2} \end{aligned}$$

$$\text{Hysteresis width} = V_{UT} - V_{LT}$$

$$= 10 \frac{R_1}{R_2} + 10 \frac{R_1}{R_2}$$


$$= 20 \frac{R_1}{R_2}$$

$$\text{Given that, } 20 \frac{R_1}{R_2} = 1\text{V}$$

$$\Rightarrow R_1 = \frac{1 \times R_2}{20} = \frac{1 \times 20\text{k}\Omega}{20} = 1\text{k}\Omega$$

$$\boxed{\text{So, } R_1 = 1\text{k}\Omega}$$

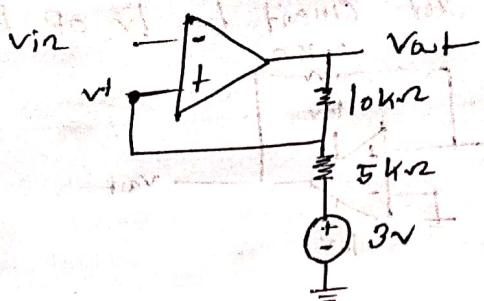Example-3
For the given op-amp. Saturation voltage are $\pm 15V$.
Find Upper and Lower threshold voltage.



SAT
Saturation means V_{out}

Solve: This is inverting Schmitt trigger.

Suppose:

$$V_{out} = +15V$$

Applying KCL,

$$\frac{v^+ - 3V}{5} = \frac{v^+ - 15V}{10} = 0$$

$$\Rightarrow 2v^+ - 6V + v^+ - 15V = 0$$

$$\Rightarrow 3v^+ = 21V$$

$$\Rightarrow v^+ = 7V$$

$$\therefore V_{UT} = 7V$$

Again, suppose, $v_{out} = -15v$

Applying KCL, $\frac{v_t - 3v}{5} + \frac{v_t + 15v}{10} = 0$

$$\Rightarrow 2v_t - 6v + v_t + 15v = 0$$

$$\Rightarrow 3v_t = -2v$$

$$\Rightarrow v_t = -\frac{2}{3}v$$

$$\therefore V_{LT} = -3v$$

~~Ans~~, $V_{UT} = 7v$

$$V_{LT} = -3v$$

$$\text{Hysteresis} = V_{UT} - V_{LT}$$

$$= 7v - (-3v)$$

$$= 7v + 3v$$

$$= 10v$$



~~Ans~~, $10v$

Non-Linear Application of Op-amp

1. By Using Op-amp draw and Explain a Schmitt trigger circuit that has zero volt centered hysteresis.

Ans:

Fig shows the Schmitt trigger

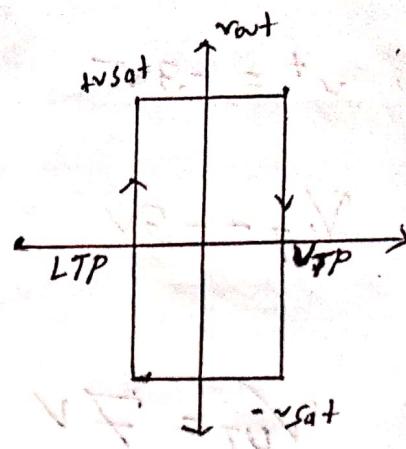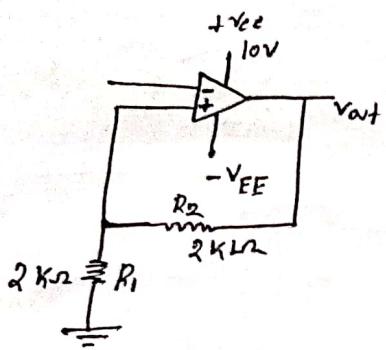

Hence,

$$V_{CC} = 10V$$

$$R_1 = R_2 = 2k\Omega$$

$$V_{cen} = 0V$$

$$\text{Feedback Fraction is, } \beta = \frac{R_1}{R_1 + R_2} = \frac{2}{2+2} = \frac{1}{2}$$

The Schmitt trigger has zero volt centered hysteresis.

The trip point are,

Assume that

$$UTP = V_{cen} + \beta V_{sat}$$

V_{sat} is 8V

$$= 0V + \frac{1}{2} \times 8$$

$$= 4V$$

$$LTP = V_{cen} - \beta V_{rat}$$

$$= 0 - \frac{1}{2}x\delta$$

$$= -4V$$

For the positive saturated output, Non-inverting input is equal to the UTP


8 .. " negative " " " " " " " " " " to store
LTP

~~Schmitt trigger:~~ To Aroid Noise Schmitt trigger is used.

Schmitt trigger is a comparison with hysteresis.

② By Using OP-Amp draw & explain a Schmitt trigger Circuit that has $\pm 5V$ Centered hysteresis;

Ans: Fig shows a Schmitt trigger circuit

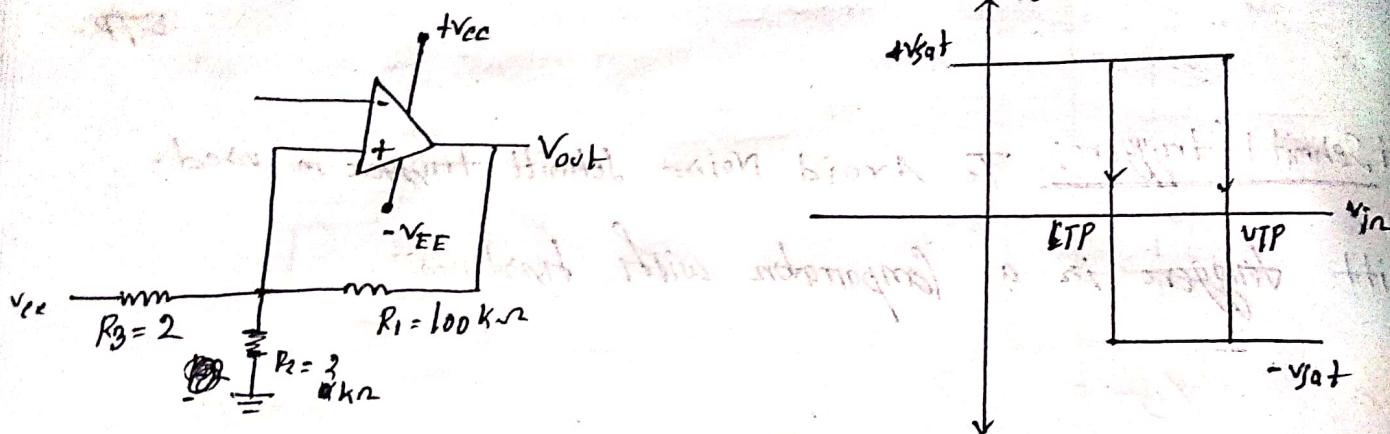

An additional resistor R_3 is connected between the non-inverting input & $+V_{cc}$. The centre of the hysteresis loop is -

$$V_{cen} = \frac{R_2}{R_2 + R_3} V_{cc}$$

$$\Rightarrow 5 = \frac{2}{2+2} V_{cc}$$

$$\Rightarrow V_{cc} = 10V$$

$$\text{The feedback fraction is } \beta = \frac{R_2 || R_3}{R_1 + R_2 || R_3} = \frac{2||2}{100+2||2} = \frac{1}{100+1} = \frac{1}{101} \approx 0.01$$

The trip points

$$V_{TP} = V_{cen} + \beta V_{sat} = 5 + 0.01 \times 10 = 5.1V$$


$$L_{TP} = V_{cen} - \beta V_{sat} = 5 - 0.01 \times 10 = 4.9V$$

Hysteresis: In a Schmitt trigger, the difference between the two trip points is called hysteresis.

Upward trip = V_{TP}

Downward trip = L_{TP}

switched logic

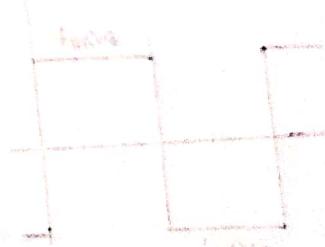

Upward trip, the input voltage is large.

switched logic

3. By Using Op-Amp draw and explain a Schmitt trigger circuit to

produce ~~triangle~~ rectangular wave from sine wave.

Ans:

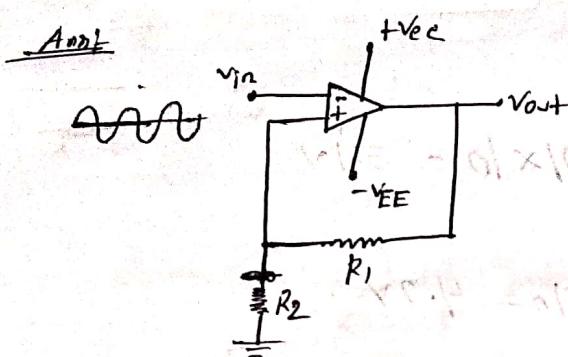


Fig: a


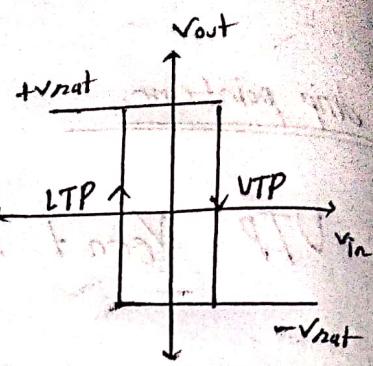


Fig: b

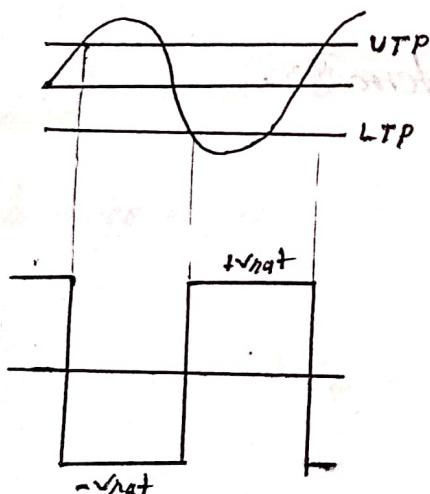

Here,

fig: a = Schmitt trigger

fig: b = Transfer characteristics

fig: c = Output voltage v_{out}

input voltage

Fig: c

⇒ When the input signal is periodic, the output of Schmitt trigger produces a rectangular waveform.

- If the input signal less than UTP the output remain High
 - As soon as input signal crosses UTP then output will become Low and it remain low until it crosses LTP.
 - As soon as input signal crosses LTP then output will become High and it remain High until it crosses UTP.



4. By using op-amp circuit and explain a Schmidt trigger circuit to produce triangular wave from rectangular wave.

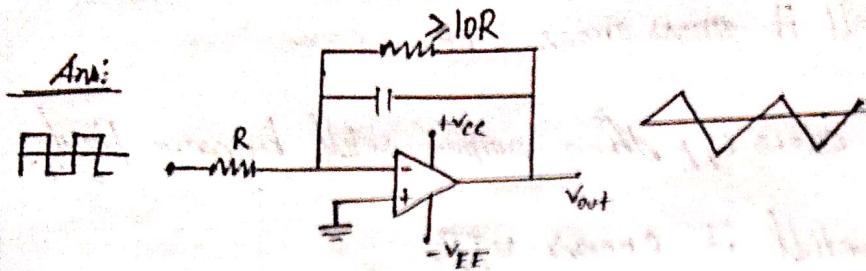


Fig: a

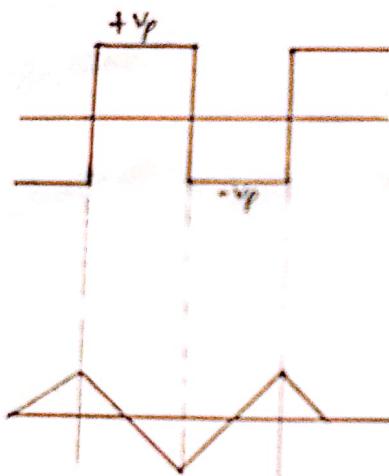


Fig: b


Fig: a \rightarrow rectangular input to integrator produces triangular input.

Fig: b \rightarrow Input output waveforms.

Fig(a) Rectangular wave to an integrator. Since the input signal has a dc or average value of zero. The dc average value of the output is also zero.

Fig(b). The Triangular wave is decreasing when the rectangular wave is increasing.

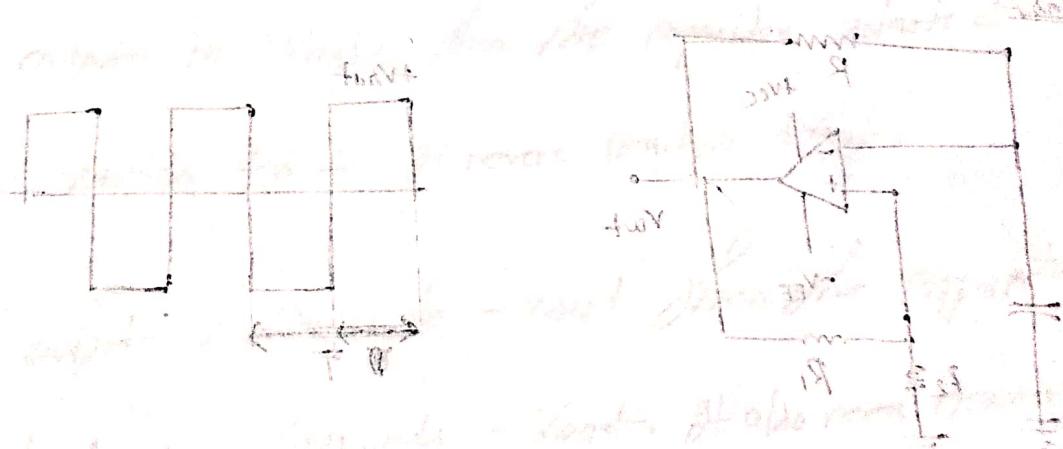→ The triangular wave is increasing when the rectangular wave is decreasing.



Oscillator: It's an electronic circuit that produces a periodic oscillating electronic signal, often a sine or square wave.

→ Convert DC to AC

⇒ 2 types of Oscillator:

• Harmonic → Sinusoidal Output

• Relaxation → Non-Sinusoidal Output

6. By Using Op-amp Draw and Explain a Relaxation Oscillator:

Anni


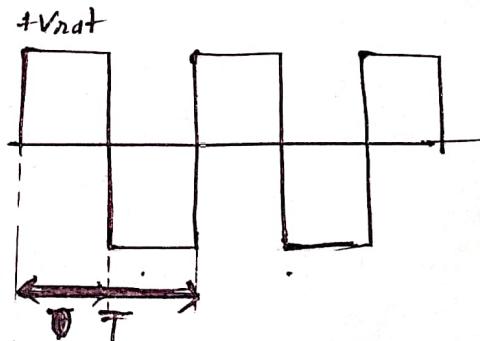
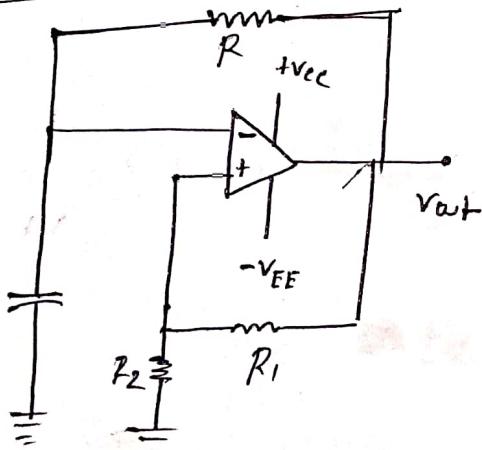


Fig: Relaxation Oscillator

Figure a shows a relaxation oscillator that has no input signal but generates an output rectangular wave.

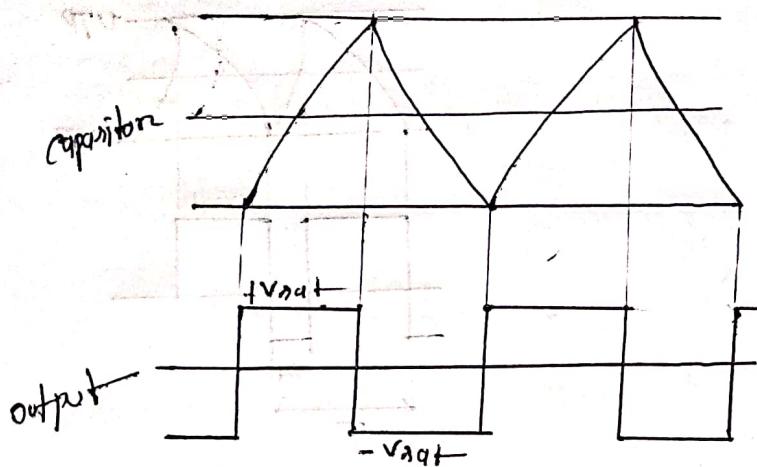Output signal frequency depends on the charging and discharging of a capacitor or inductor.




When the output is $+V_{sat}$, then the capacitor starts to


change towards $+V_{sat}$. It never reaches $+V_{sat}$.

When the output switches to $-V_{sat}$ then the capacitor starts discharging towards $-V_{sat}$. It also never reaches $-V_{sat}$.

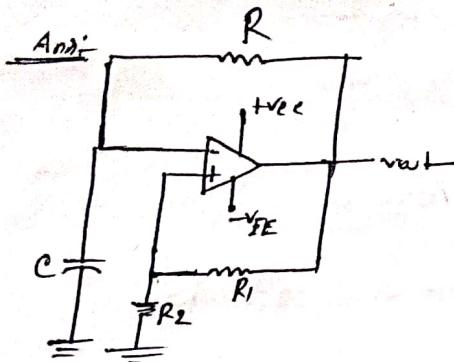To prove that, $T = 2RC \ln \frac{1+\beta}{1-\beta}$ is the period of the output rectangular wave of an op-amp relaxation oscillator, where β = feedback fraction.



Fig(a): Relaxation Oscillator

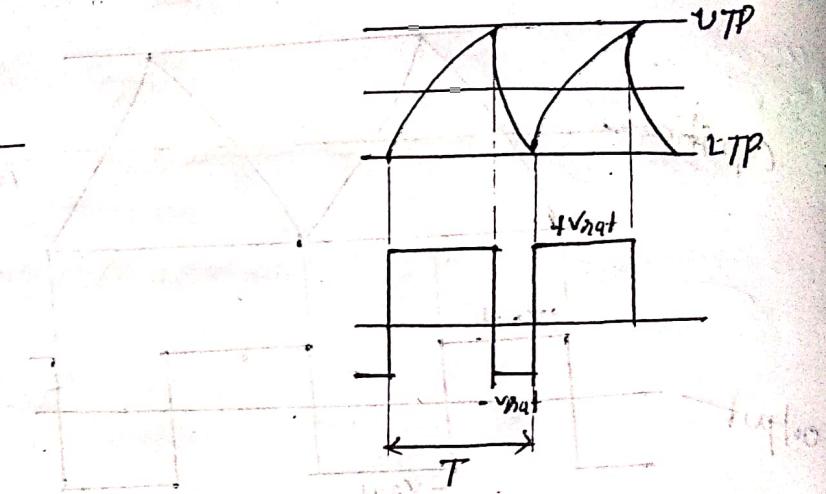

Fig(b): Capacitor & output voltage

Figure shows that V_{TP} has a value of $+BV_{sat}$ &

$$V_{LP} \text{ " " " } -\beta V_{sat}$$

We get,

$$V = V_i + (V_p - V_i) \left(1 - e^{-t/R_e} \right) \rightarrow (i)$$

where, V = Capacitor voltage

t = changing time

V_i = Initial capacitor voltage

V_p = Target " "

The capacitor charge starts with an initial value $-\beta V_{sat}$ & ends with a value $+\beta V_{sat}$

So hence,

$$v_i = -\beta V_{sat}$$

$$v_f = +V_{sat}$$

$$v = \beta V_{sat}$$

so from eqn (i) \Rightarrow

$$v = v_i + (v_f - v_i) (1 - e^{-t/Rc})$$

$$\Rightarrow \beta V_{sat} = -\beta V_{sat} + (V_{sat} + \beta V_{sat}) (1 - e^{-T/2Rc})$$

$$\Rightarrow 2\beta V_{sat} = V_{sat} (1 + \beta) (1 - e^{-T/2Rc})$$

$$\Rightarrow 2\beta = (1 + \beta) (1 - e^{-T/2Rc})$$

$$\Rightarrow \frac{2\beta}{1 + \beta} = 1 - e^{-T/2Rc}$$

$$\Rightarrow e^{-T/2Rc} = 1 - \frac{2\beta}{1 + \beta}$$

$$\Rightarrow e^{-T/2Rc} = \frac{1 + \beta - 2\beta}{1 + \beta} = \frac{1 - \beta}{1 + \beta}$$

$$\Rightarrow -T/2Rc = \ln \left(\frac{1 - \beta}{1 + \beta} \right)$$

Picto

$$\Rightarrow -T = 2RC \ln\left(\frac{1+\beta}{1-\beta}\right)$$

$$\Rightarrow -T = 2RC \cdot \frac{1}{\alpha} \left(\frac{HO}{FB} \right)$$

$$\therefore T = 2RC / \alpha \left(\frac{1+\beta}{1-\beta} \right) \quad \boxed{\text{Proved}}$$

⑧ An op-amp relaxation oscillator has feedback insertion $\beta = 0.2$. Feedback resistor $R = 4.7$ ohms & charging-discharging capacitor $C = 0.022 \mu F$. What is the frequency of the output voltage in Hz?

Ans: Given that, $R = 4.7 \Omega$, $\beta = 0.2$

$$C = 0.022 \mu F$$

$$f = ?$$

$$T = 2RC \ln \frac{1+\beta}{1-\beta}$$

$$= 2 \times 4.7 \times 0.022 \times \ln \left(\frac{1+0.2}{1-0.2} \right)$$

$$= 0.6089 s$$

$$\therefore \text{Frequency } f = \frac{1}{T}$$

$$= \frac{1}{0.6089}$$

$$= 1.6423 \text{ Hz}$$

Q. Draw and Explain a practical op-amp integrator. Explain the necessity of large resistor across the capacitor.

Ans:

An integrator produce an output voltage that is proportional to the waveform of the input.


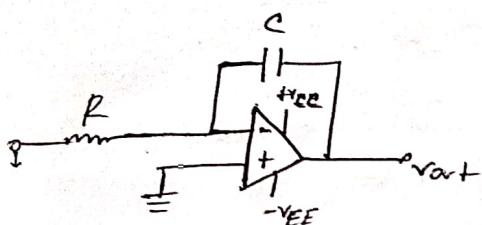


Fig. a Integrator

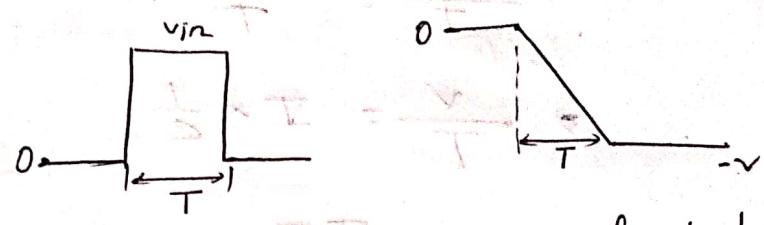

(b) typically input is
rectangular wave

(c) Typical output

Because of virtual ground, the input current is constant & equals.

$$I_{in} \cong \frac{v_{in}}{R}$$

approximately all current goes to the capacitor.

$$C = \frac{Q}{V}$$

$$\therefore V = \frac{Q}{C} \rightarrow (i)$$

Since constant current is flowing into the capacitor
charge Q increasing linearly.

P. JIO

By dividing the equation (2) by T_1 :

$$\frac{V}{T} = \frac{\alpha/c}{T}$$

$$\Rightarrow \frac{V}{T} = \frac{\alpha}{c} \times \frac{1}{T}$$

$$\Rightarrow \frac{V}{T} = \frac{\alpha}{T} \times \frac{1}{c}$$

$$\Rightarrow \frac{V}{T} = I \times \frac{1}{c}$$

$$\Rightarrow V = \frac{IT}{c}$$

where,

V = Capacitor voltage


I = Charging Current

T = Charging Time

C = Capacitor

Necessity of large resistor across the capacitor:

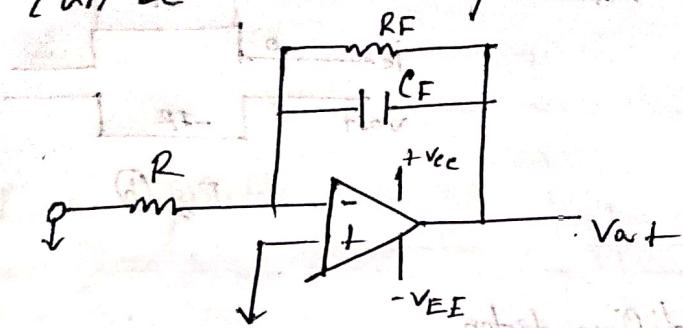→ To Avoid the saturation of the Output voltage and provide gain. (Contrary), a resistor with large value of resistance can be added in parallel with the Capacitor.



⑩ Draw and Explain a practical op-amp differentiator. Explain the necessity of a small resistor in series with the capacitor.

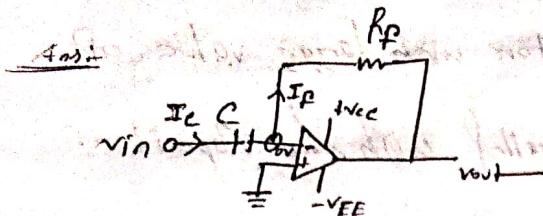


Fig: (a)

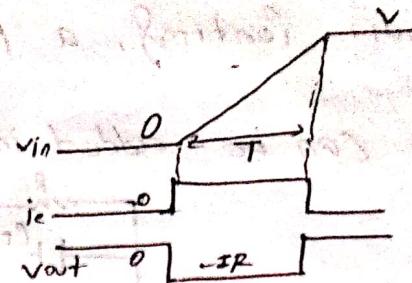


Fig: (b)

Fig (a) shows an op-amp differentiator

Current I_C flowing through this capacitor and

current I_F " " " R_F and producing a voltage. This voltage is proportional to the slope of the input voltage.

The op-amp is an ideal op-amp. That's why no current flows inside this op-amp.

The capacitor voltage is -

$$V = \frac{Q}{C}$$

Dividing both sides by time T ,

$$\Rightarrow \frac{v}{T} = \frac{Q/T}{C}$$

$$\therefore v = \frac{IT}{C}$$

$$\Rightarrow I = \frac{Cv}{T}$$

where,

I = Capacitor current

C = Capacitance


v = voltage at end of op-amp

T = time between start and end of op-amp.



in Capacitor Discharge

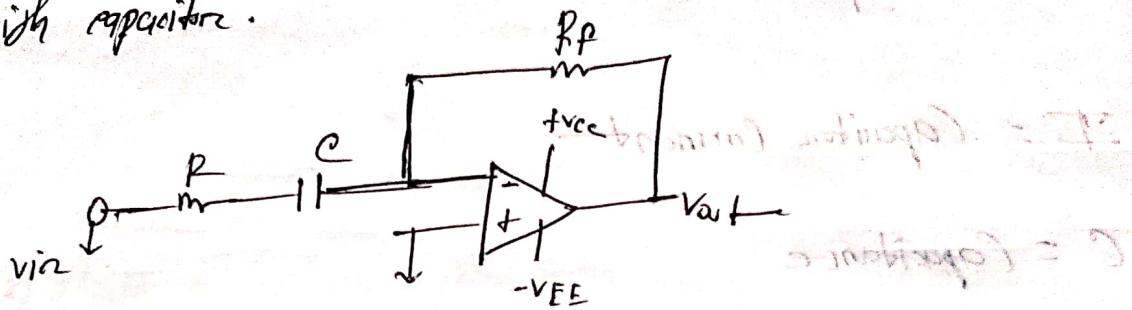- # The necessity of small resistor in series with capacitor:
- As the frequency will ~~increase~~ increase the input impedance of the circuit will reduce.
 - To solve this problem a small resistor is added with capacitor.



- going to low to negative = V_{EE}
 - going to low bias voltage generated with $\frac{R_f}{R_f + R}$

Multivibrator

Chandler - All About Electronics

Multivibrator

- ⇒ The Multivibrator is the electronic circuit which is used to implement two state devices like Oscillator, Timer and Flip-Flop.
- ⇒ Two state means two voltage level


High & Low

3 types

- Monostable Multivibrator → One stable state
One unstable state
- Astable Multivibrator → Both are unstable state
- Bistable Multivibrator → Both are stable state


Astable Multivibrator:

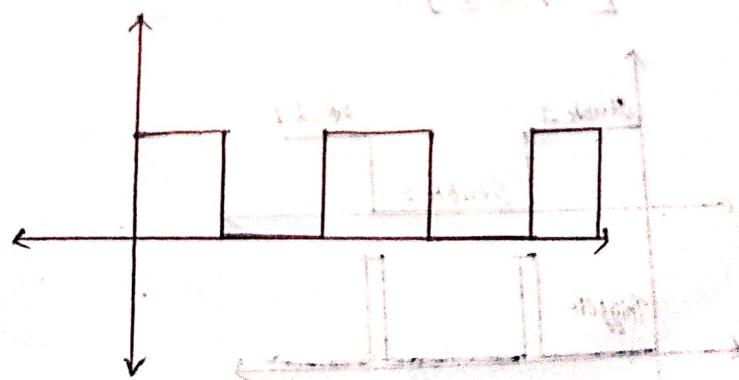- Both are Unstable States at any time
- Used in Relaxation Oscillator




Monostable Multivibrator

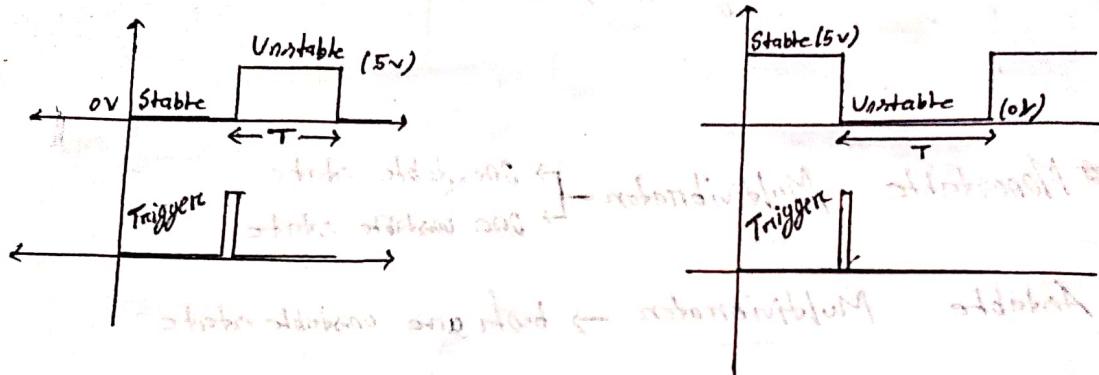- One stable state
 ↳ One unstable state
 → output remain in the stable state.
- When external trigger applied output goes to unstable state.
- Widely used in [Timer]




Bistable Multivibrator:

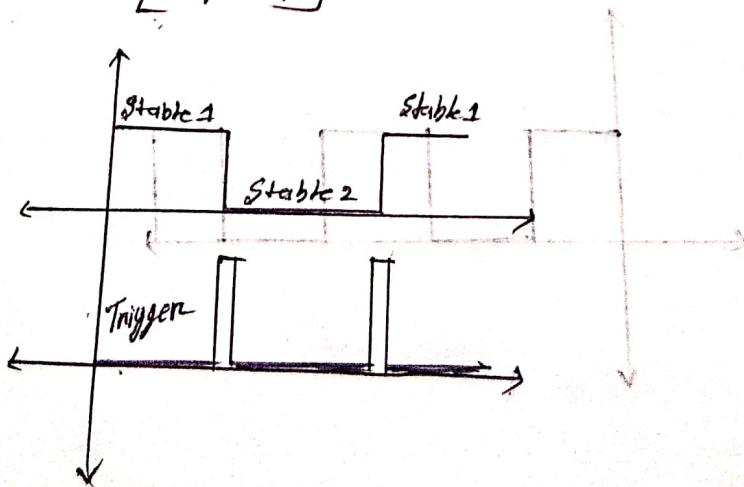- Both states are stable ~~not~~ states
- Whenever trigger applied output goes to one stable to another stable state.
- Widely used in [Flip-Flop]




Introduction to 555 Timer

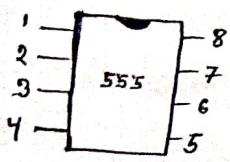

1 → Ground
2 → Trigger
3 → Output
4 → Reset

8 → V_{cc}
7 → Discharge
6 → Threshold
5 → Control



G T O R
C T D V

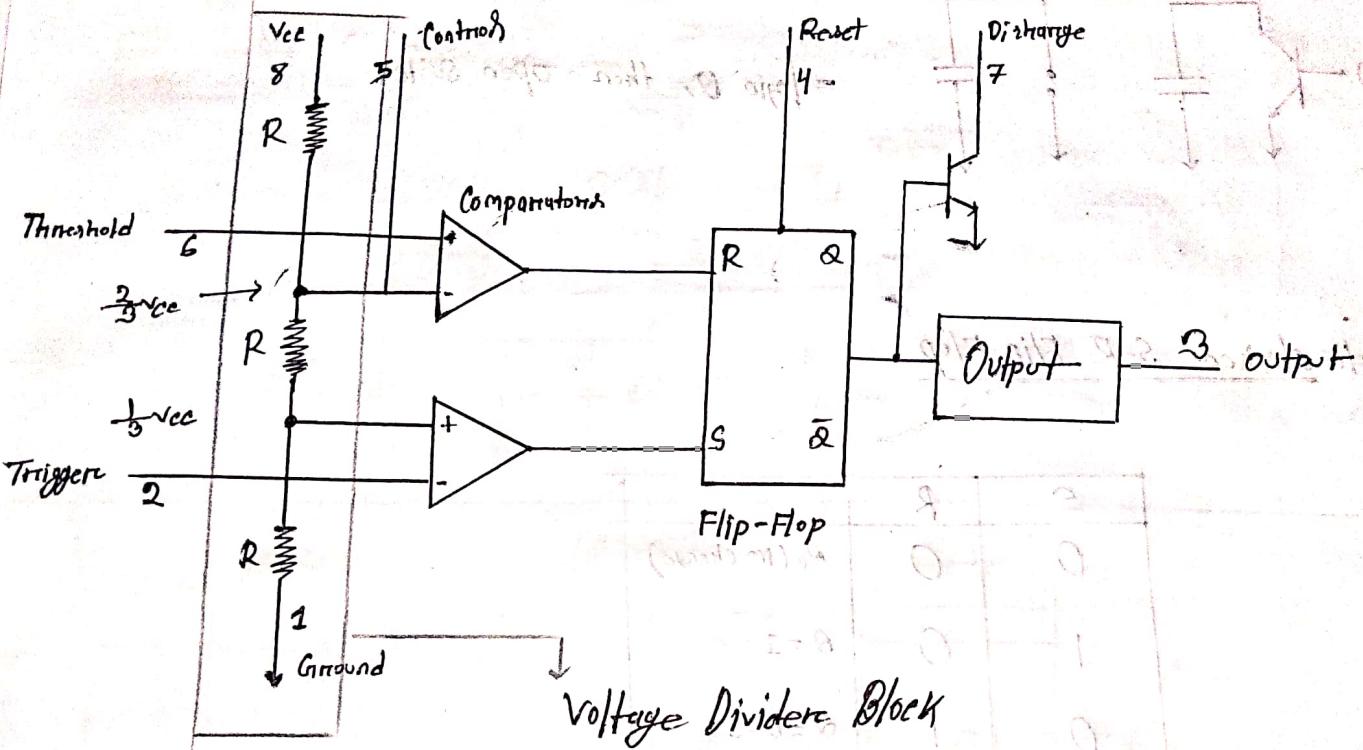



Pin 8 → Supply Voltage Pin 4.5V to 15V.

$\frac{2}{3} V_{cc}$ → High Voltage

$\frac{1}{3} V_{cc}$ → Low Voltage

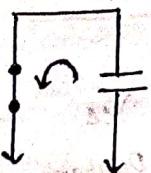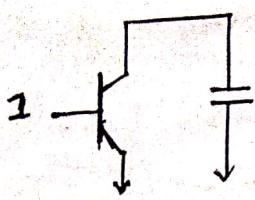

\Rightarrow logic 1, then close switch

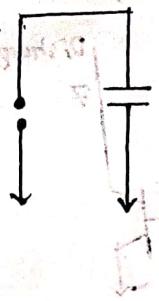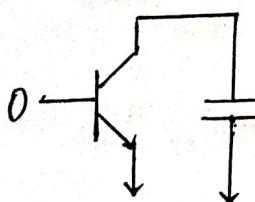



\Rightarrow logic 0, then open switch

clocked S-R Flip Flop

S	R	Q (No change)
0	0	$Q = 0$
1	0	$Q = 1$
0	1	$Q = 0$
1	1	Invalid


555 timer as Monostable Multivibrator

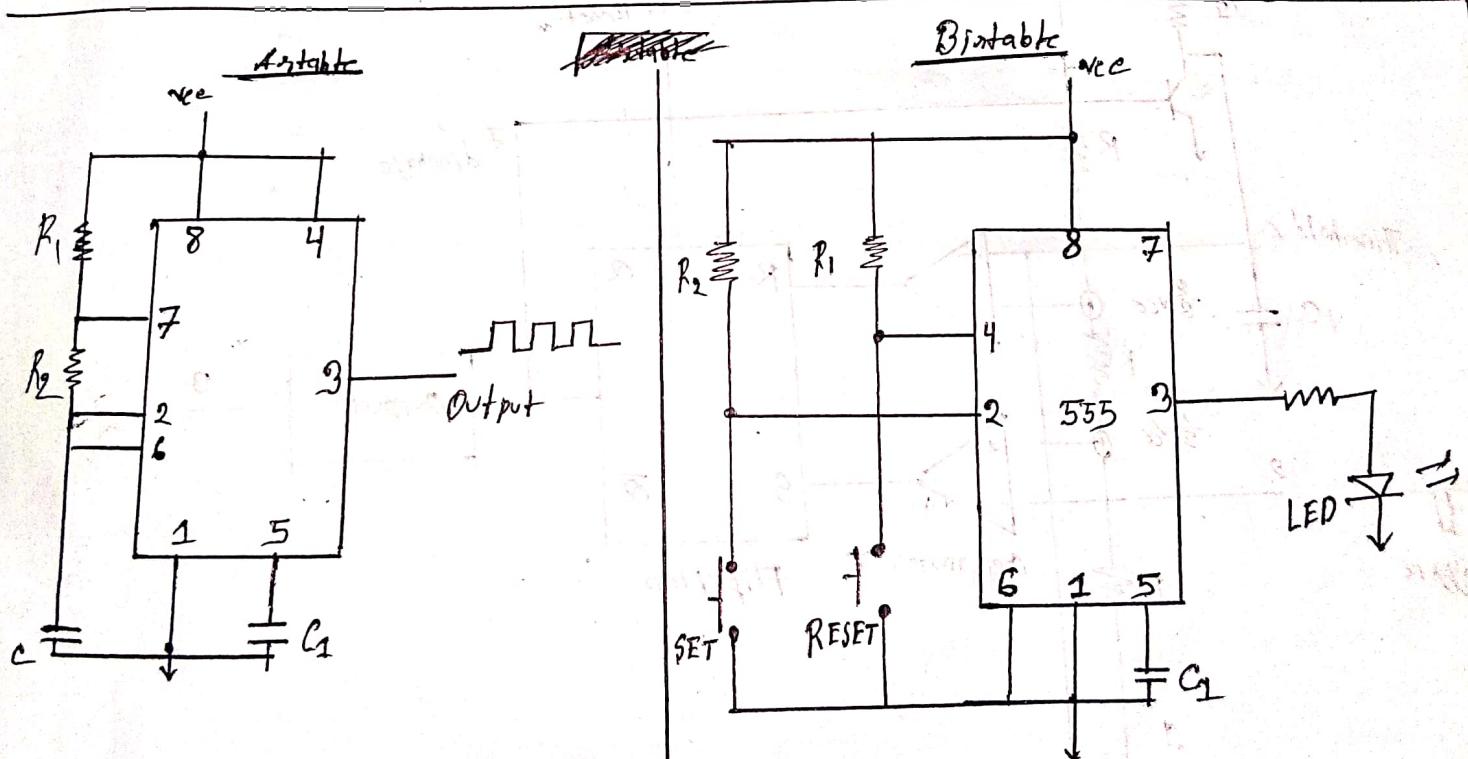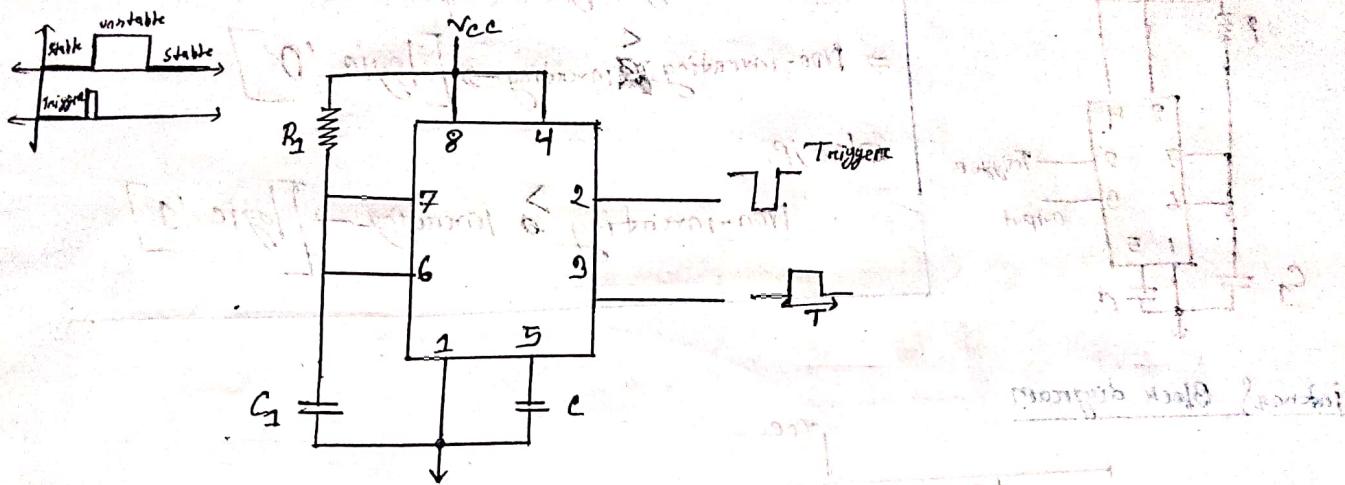- One stable state
- One unstable state
- whenever a trigger signal is applied then the stable state goes into unstable state.



555 Timer as Monostable Multivibrator


Note:

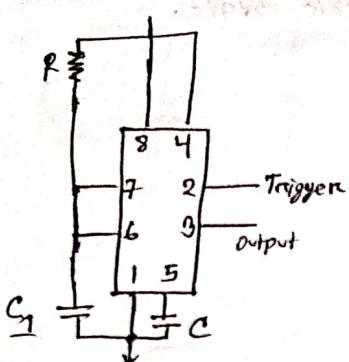

Condition Voltage
 • If, inventing Node \wedge more than Non-inverting
 Node voltage, Then comparitor output will be
 \Rightarrow Non-inverting \leq inventing \rightarrow [Logic '0']

else if,
 Non-inverting $>$ inventing \rightarrow [Logic '1']

internal Block diagram

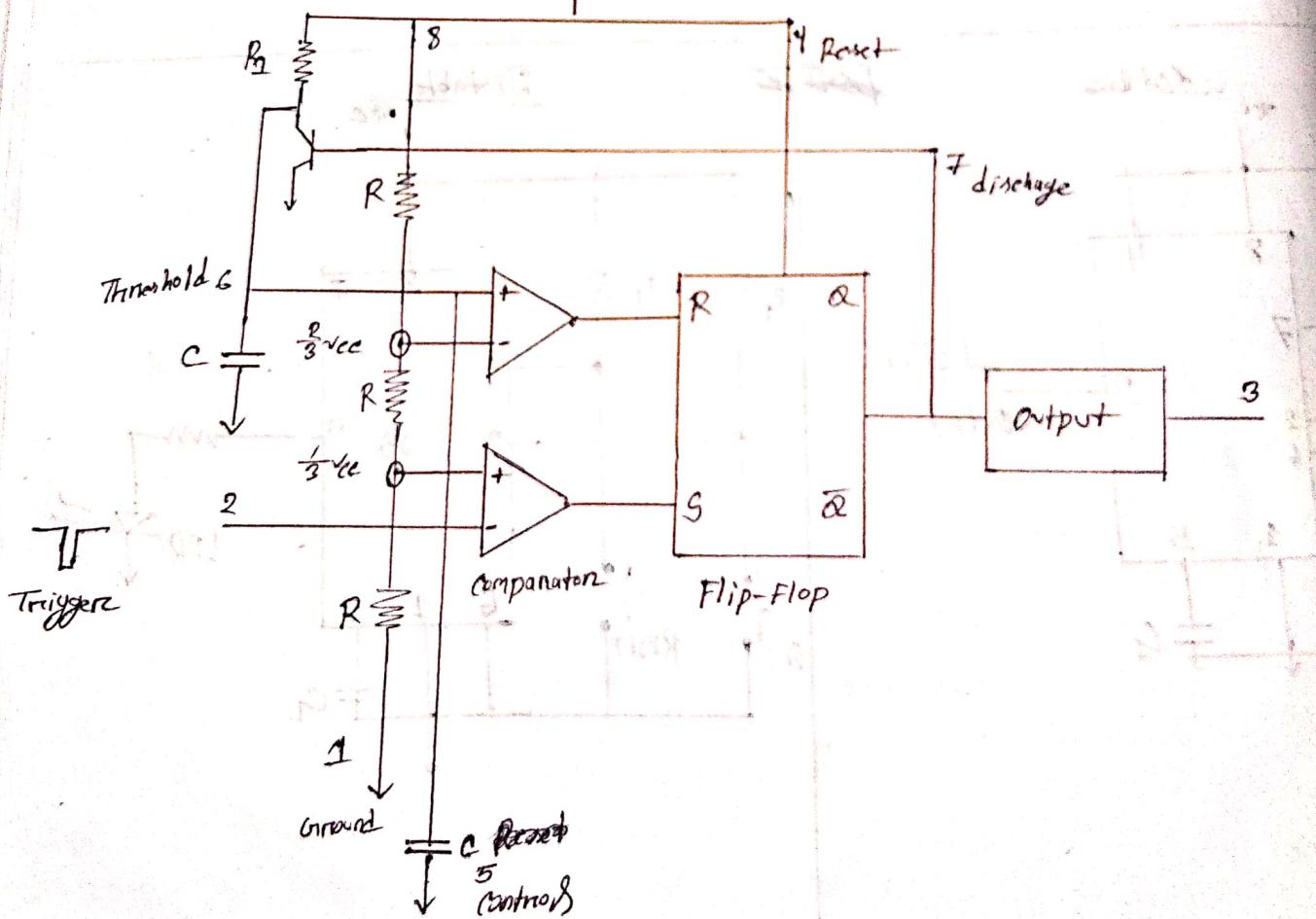

Working Procedure

⇒ When the output = 0, then $Q = 0$, $\bar{Q} = 1$

Ans. $\bar{Q} = 1$, then the transistor ON

⇒ When the Pin 6 is ground potential, Then voltage at pin 6 $< \frac{2}{3} V_{CC}$

So, the 1st comparator output logic '0'

At the 2nd comparator,

trigger is not applied, then pin 2 at V_{CC} voltage.

Then voltage at pin 2 $> \frac{1}{3} V_{CC}$

So, the 2nd comparator output logic ~~'0'~~ '0'

Hence,

$$S = 0 \quad R = 0, \quad Q = 0 \quad \bar{Q} = 1$$

⇒ Whenever the trigger is applied,

then voltage at pin 2 $< \frac{1}{3} V_{CC}$

So, the 2nd comparator output logic '1'

During triggering action $\bar{Q} = 1$ - so this pin 6 remain at ground potential.

So, the output of 1st comparator remains same.

Hence,

$$S = 1, \quad R = 0, \quad Q = 1 \quad \bar{Q} = 0$$


As soon as $Q = 0$ the transistor switch off.

And now capacitor C_1 start charging through V_{CC} .


⇒ After the triggering action, once again output of the 2nd comparitor will logic '0'

Now, during charging capacitor, the voltage at pin 6, just $\frac{2}{3} V_{CC}$ voltage, the output of 1st comparitor logic '1'
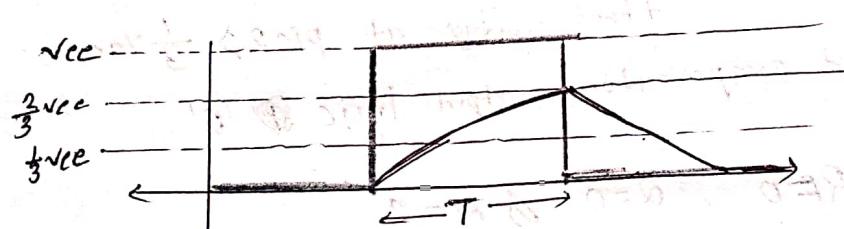
$$R = 1, S = 0 \quad Q = 0, \bar{Q} = 1$$



555 timer An Astable Multivibrator

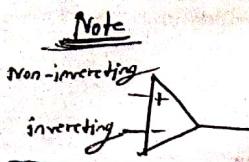

Condition



if Non-inverting voltage < inverting voltage

[logic '0']


else if,

Non-inverting voltage > inverting voltage [logic '1']


- Both state are unstable state

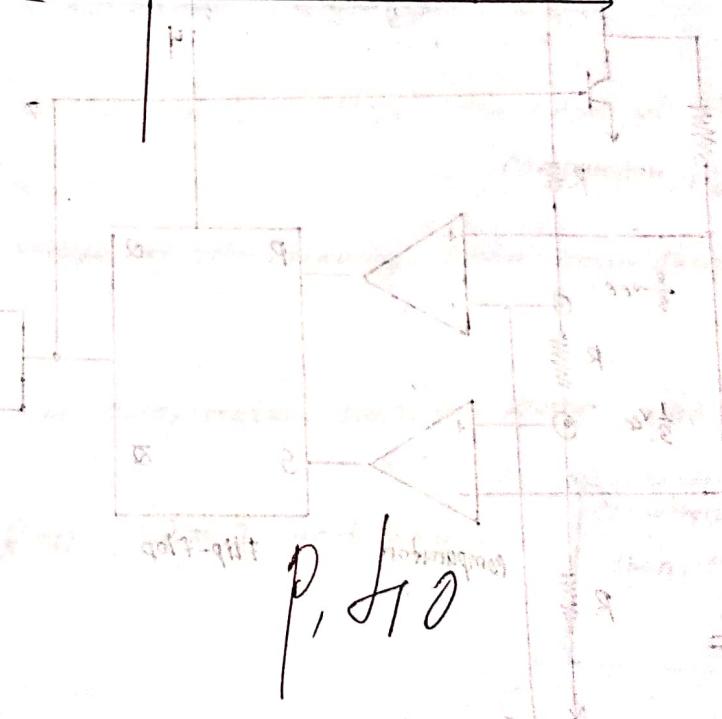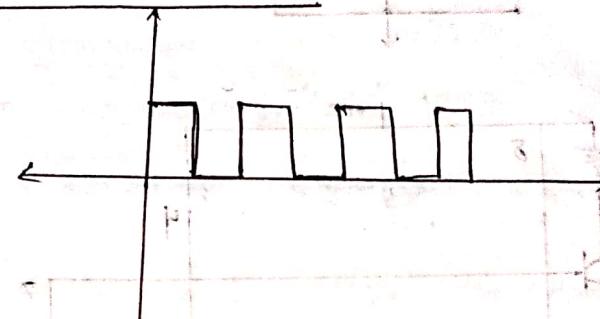

P, J, O

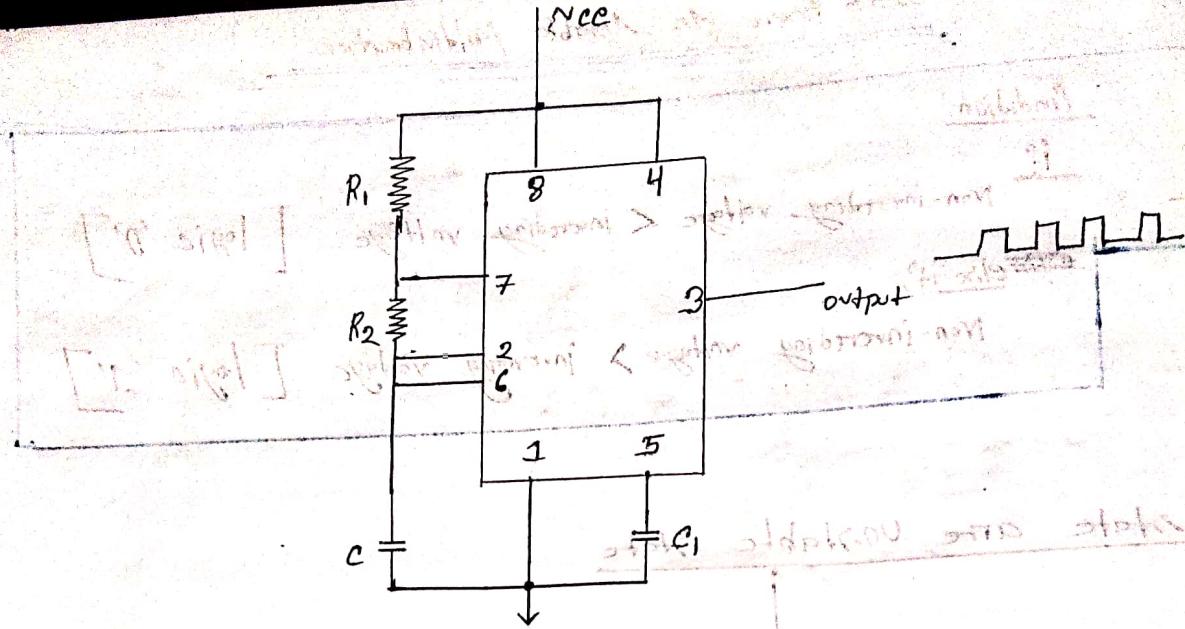

Block Diagram

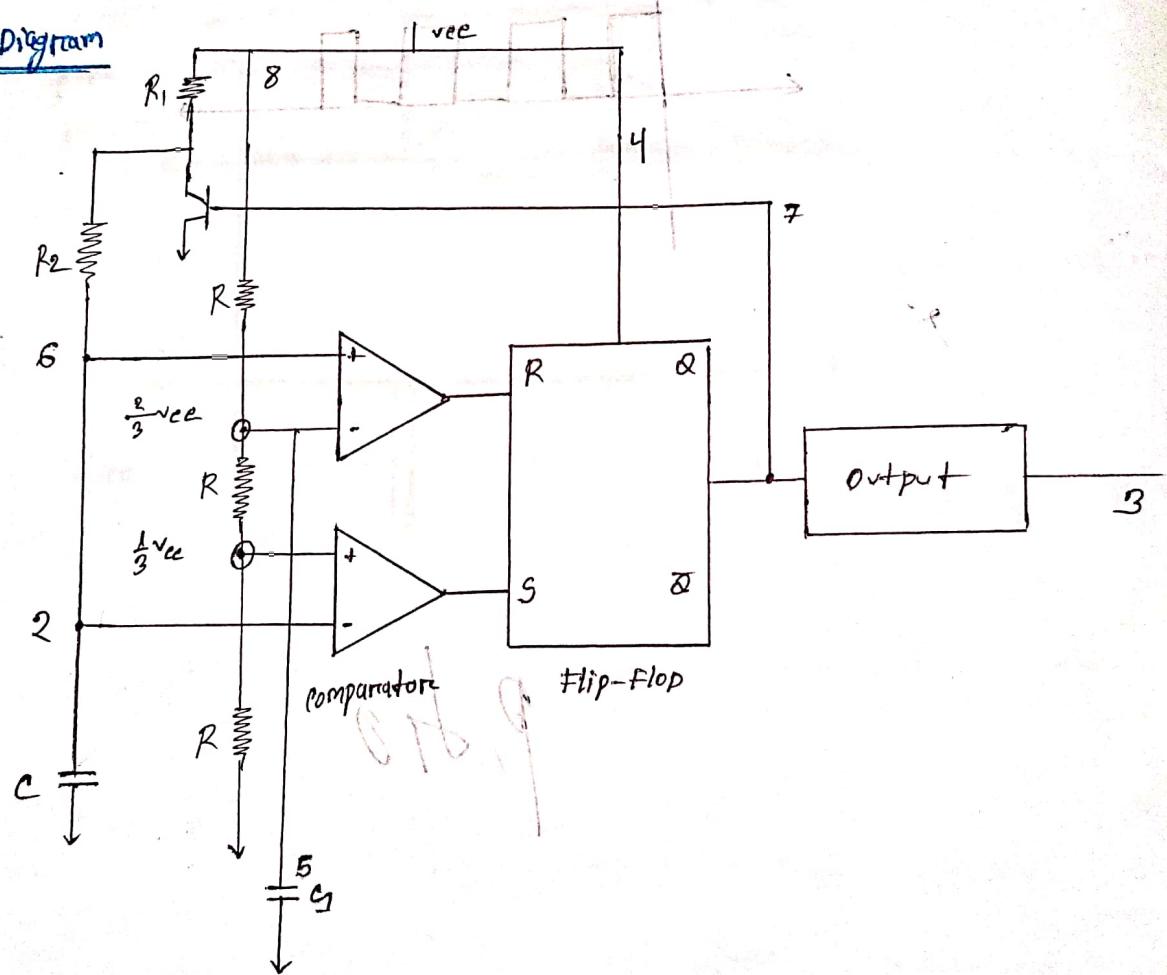

\Rightarrow For 1st comparator, initially the voltage at the inverting node more than voltage at non-inverting Node.

So, 1st comparator output logic '0'

For 2nd comparator, initially the voltage at the inverting node less than voltage at non-inverting Node.

So, 2nd comparator output logic '1'

Hence, $S=1$, $R=0$, $Q=1$ and $\bar{Q}=0$

As soon as $\bar{Q}=0$, the transistor switch off.

so, the capacitor C start charging through R_1 and R_2 gradually.

and the voltage pin 2 and 6 start increasing.

\Rightarrow Whenever, pin 2 voltage crosses $\frac{1}{2}$ Vcc voltage, the output of the 2nd comparator logic '0'

Because at that time the voltage at the inverting Node more than the voltage at Non-inverting Node.

while, output of the 1st comparator remain same logic '0'

Hence,

$S=0$, $R=0$, $Q=1$ and $\bar{Q}=0$.

as, when $S=0$, $R=0$
then, Q will remain
same
Node.

\Rightarrow Whenever, pin 6 voltage Cross $\frac{2}{3}$ Vcc voltage, the output of the 1st comparator logic '1'

Because at that time the voltage at the inverting Node less than the voltage at Non-inverting Node.

while, output of the 2nd comparator remain same logic '0'

Hence,
 $S=0$, ~~$R=1$~~

$Q=0 \& \bar{Q}=1$

As soon as $\bar{Q}=1$, then the transistor ON

the capacitor C start discharging through the transistor.

\Rightarrow When the voltage at pin 6 $< \frac{2}{3}V_{cc}$, then the output of the 1st comparator logic '0'

2nd comparator output remain same logic '0'

Hence,


$S=0$, $R=0$, $Q=0$ & $\bar{Q}=1$

\Rightarrow Whenever the voltage at pin 2 $< \frac{1}{3}V_{cc}$, then the output of the 2nd comparator logic '1'

1st comparator output remain same logic $R=0$

$S=1$, $R=0$, $Q=1$ & $\bar{Q}=0$

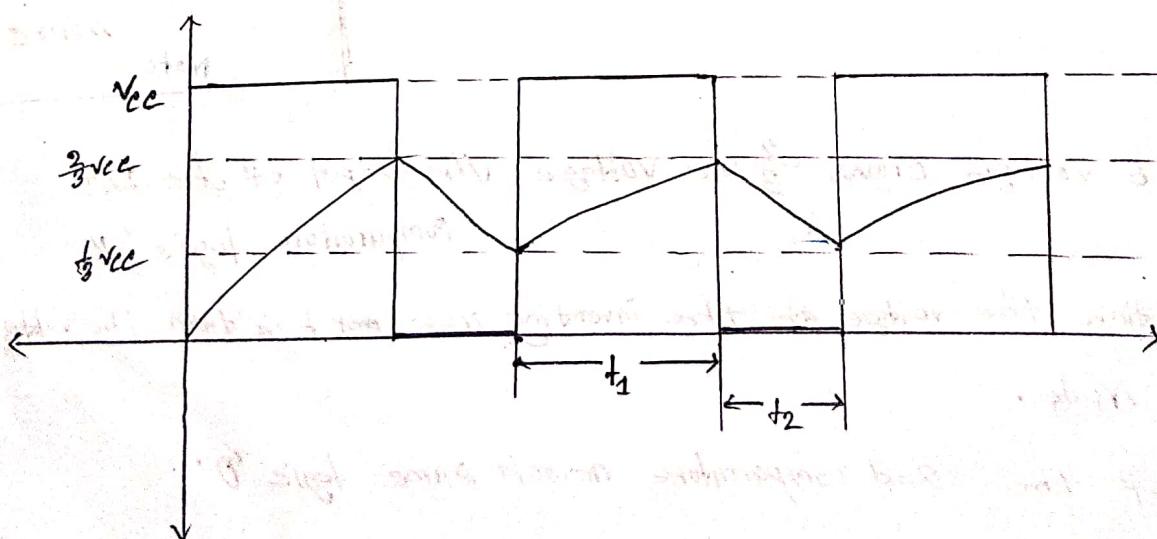As soon as $\bar{Q}=0$, the transistor will get OFF. The capacitor again charging through R_1 and R_2 .



$t_1 \rightarrow$ Charge through R_1 & R_2 $\frac{1}{3} V_{cc}$ to $\frac{2}{3} V_{cc}$ voltage.

$t_2 \rightarrow$ discharge $\therefore R_2 \frac{2}{3} V_{cc}$ to $\frac{1}{3} V_{cc}$ voltage

So,

$$t_1 = 0.693(R_1 + R_2)C$$

$$t_2 = 0.693 R_2 C$$

$$\boxed{t_1 > t_2}$$

Total time,

$$T = t_1 + t_2$$

$$= 0.693(R_1 + R_2) + 0.693 R_2$$

$$= 0.693(R_1 + 2R_2)C$$

Duty cycle,

$$= \frac{\text{On time pulse}}{\text{Total time}}$$

$$= \frac{t_1}{T} = \frac{0.693(R_1 + R_2)}{0.693(R_1 + 2R_2)}$$

$$\boxed{\text{Duty cycle} = \frac{R_1 + R_2}{R_1 + 2R_2}}$$

That's why the Duty cycle more than the 50%

\Rightarrow To get 50% cycle the value of R_1 should be zero,

when, $R_1 = 0$, Then Duty cycle = $\frac{R_2}{2R_2} = \frac{1}{2} = 50\%$


555 timer as Bistable Multivibrator

Note:


Condition

- Condition

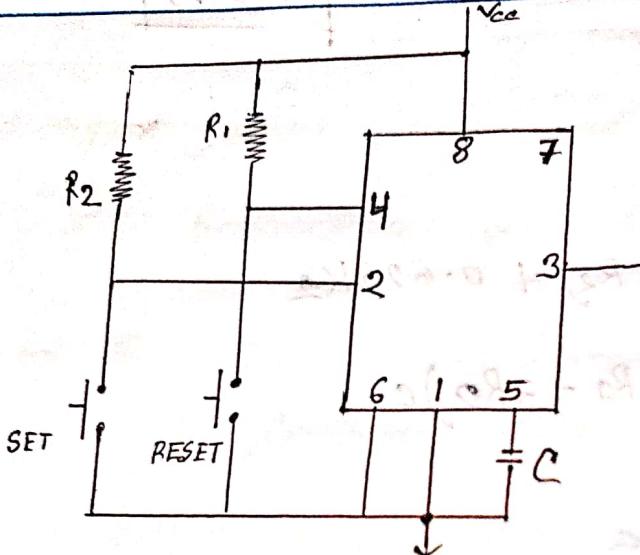 - if, Non-inverting \geq inverting [logie '0']
 - else if, non-inverting $>$ inverting [logie '1']



Block Diagram

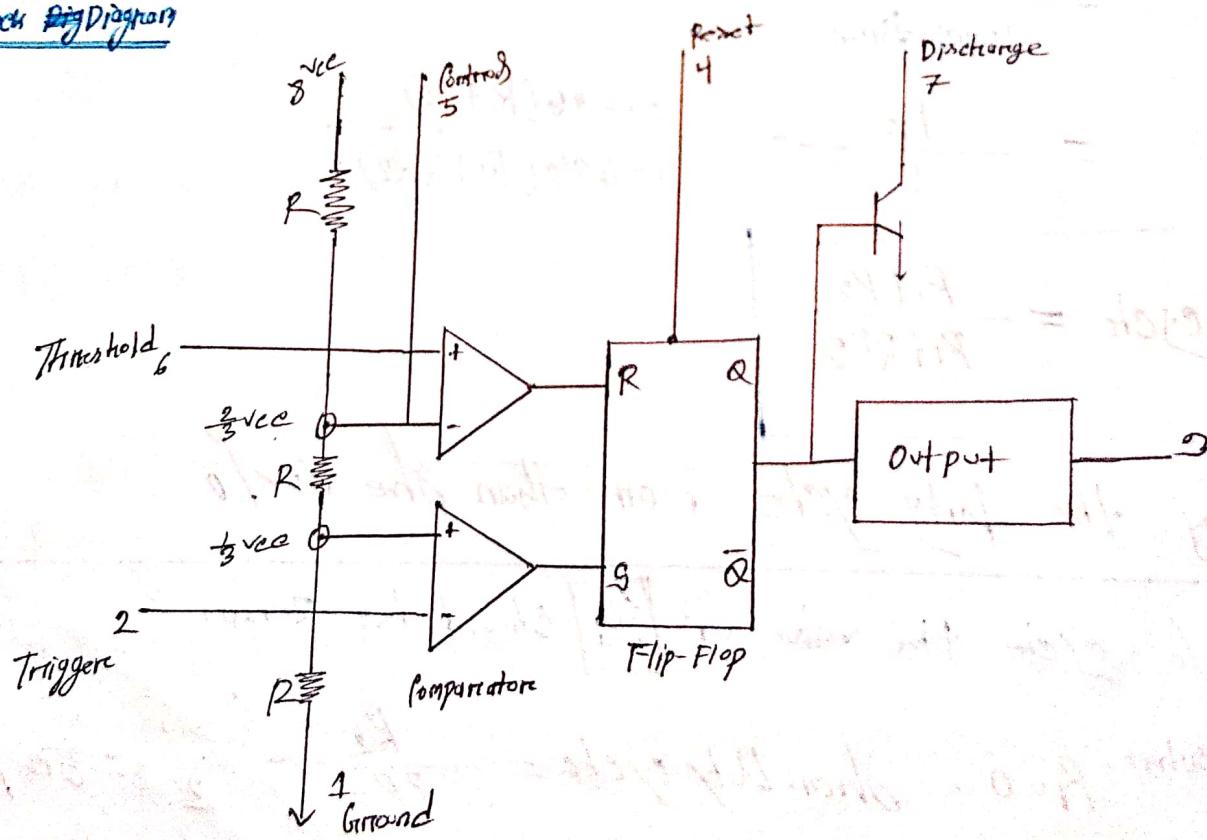

Working Procedure: $\frac{2}{3}V_{cc}$ & $\frac{1}{3}V_{cc}$ are reference voltage

⇒ Threshold voltage connected to ground, that's why voltage at node 6 $< \frac{2}{3}V_{cc}$ voltage

So, the 1st comparator output logic '0'

The trigger pin connected to the supply voltage So voltage at node 2 $> \frac{1}{3}V_{cc}$ voltage

So, the 2nd comparator output logic '0'

Here, $S=0$ and $R=0$, $Q=0$ & $\bar{Q}=1$

⇒ When press the SET pin, then pin 2 connected to the ground potential

So, voltage at pin 2 $< \frac{1}{3}V_{cc}$ & output logic '1'

1st comparator output remain same logic '0'

Here, $S=1$ and $R=0$, $Q=1$ & $\bar{Q}=0$

⇒ Whenever trigger pin is pressed, at that time

$S=1$ and $R=0$, $Q=1$

⇒ Once the switch is released then once again voltage at pin 2 equal to supply voltage.

$S=0$ & $R=0$, $Q=1$


⇒ When press the RESET then pin 4 connected to the ground terminal,

~~Reset = 0~~ Reset = 0


$Q=0$

P. J. P.

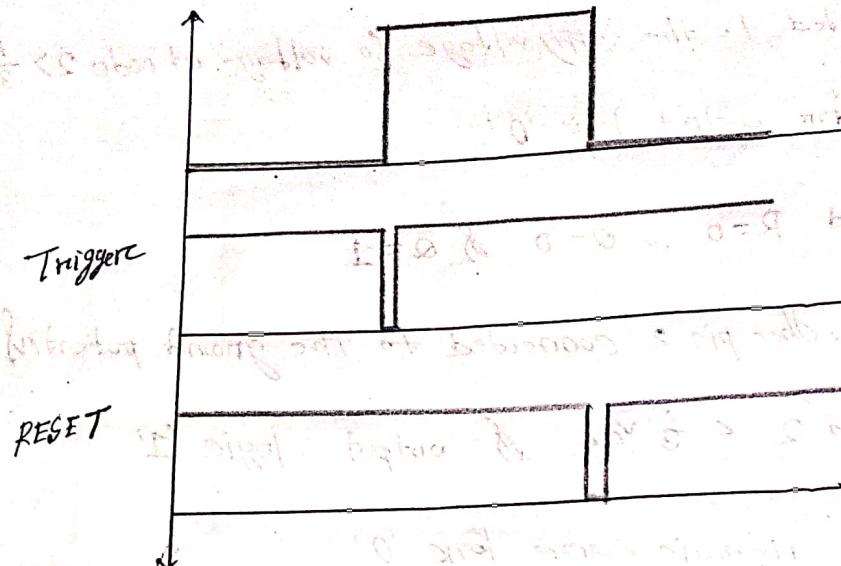→ Released the RESET Pin,
 $S=0 \& R=0, Q=0$




Note

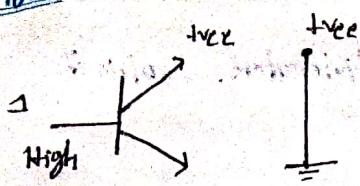

npn

- If we applied High voltage(1) in any transistor Base, then it goes to Saturation Region And start conduct.
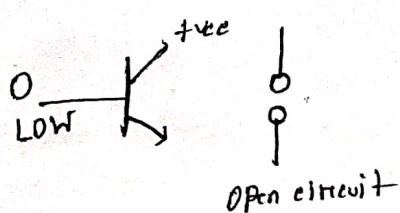
$$V_C = \downarrow \downarrow \text{ Minimum}$$



- If we Applied Low voltage(0) in any transistor Base, then it goes to Cut off state.


$$V_C = \uparrow \uparrow \text{ High}$$

p+to

npn Astable

⑯ By using two npn transistors draw an Astable Multivibrator. Explain.

Ans:-

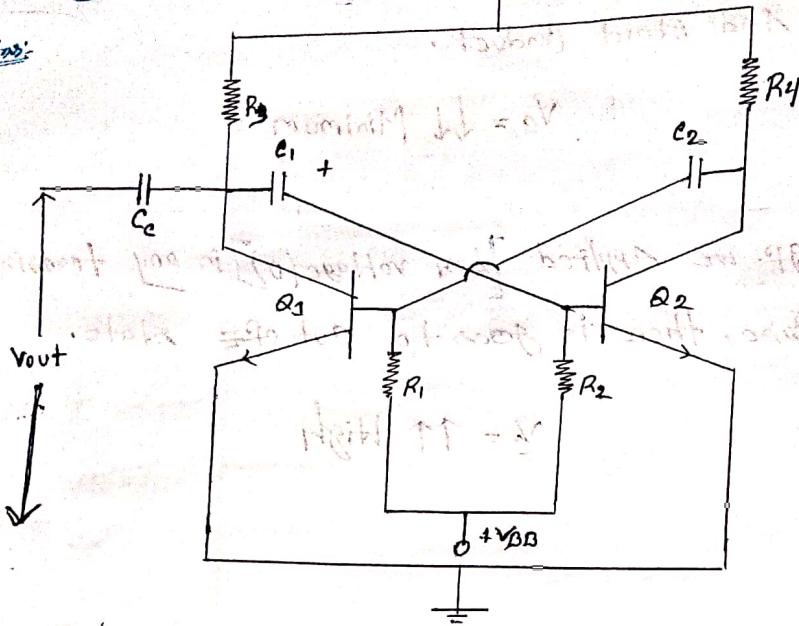

Two ~~transistors~~ $\alpha_1 \& \alpha_2$, $\alpha_1 \neq \alpha_2$

If V_{cc} start supply either α_1 or α_2 will conduct.

⇒ Assume, α_1 Conduct first, & it goes to Saturation Region.

That's why $V_c = \text{minimum } \downarrow$


⇒ Decrease voltage V_c apply to Base α_2

if we applied low voltage into Base transistors, then it goes to cut off state.

That's why $V_c = \text{High } \uparrow$


- Increases voltage applied to Base Q1
 If we applied high voltage into Base transistor, then it goes to Saturation Region, that's why $V_C = \text{minimum} \downarrow \downarrow$
- After some time Q_1 completely goes to saturation Region &
 Q_2 " " " Cut off "
- Then +V_{BB} supply current. As Q_2 is cut off region.
 The current I pass through capacitor C₁. Then Capacitor C₁ instant changing.
- The high voltage apply to Base Q2. As we know then transistor move to ~~saturation~~ region.
 That's why $V_C = \downarrow \downarrow$
- The decrease voltage V_C apply to Base Q1, then Q1 move to cut-off region.
 That's why $V_C = \uparrow \uparrow$

Output

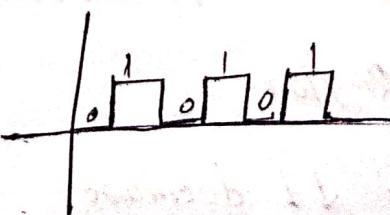

Q1 By using two npn transistors draw a Monostable Multivibrator. Explain

Ans:

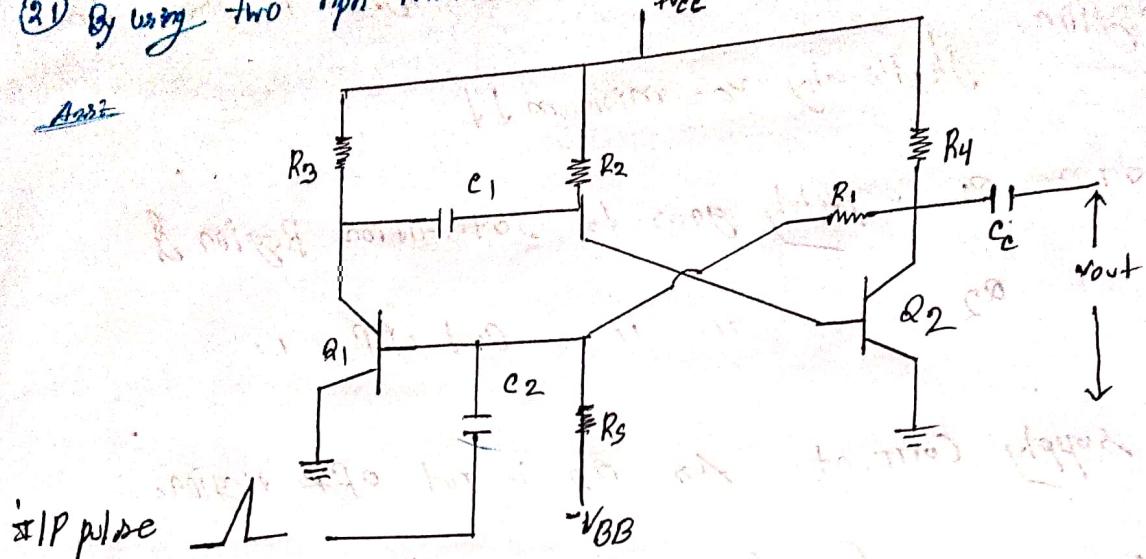

For $-V_{BB}$, transistor Q_1 goes to cut off state.

Because $-V_{BB}$ low voltage apply to the Base of Q_1 .

So, $V_C = \uparrow\uparrow$ increase.

The increase V_C voltage apply to the Base transistor Q_2 .

That's why transistor Q_2 goes to saturation Region.

So, $V_C = \downarrow\downarrow$ decrease.


Trigger \rightarrow short duration High pulse

when we trigger the circuit to transistor Q_1 , then Q_1 goes to saturation Region.

$V_C = \downarrow\downarrow$ decrease;

The decrease voltage apply to Base Q2
then Q2 goes to cut off state

so, $V_C = 11$ increase

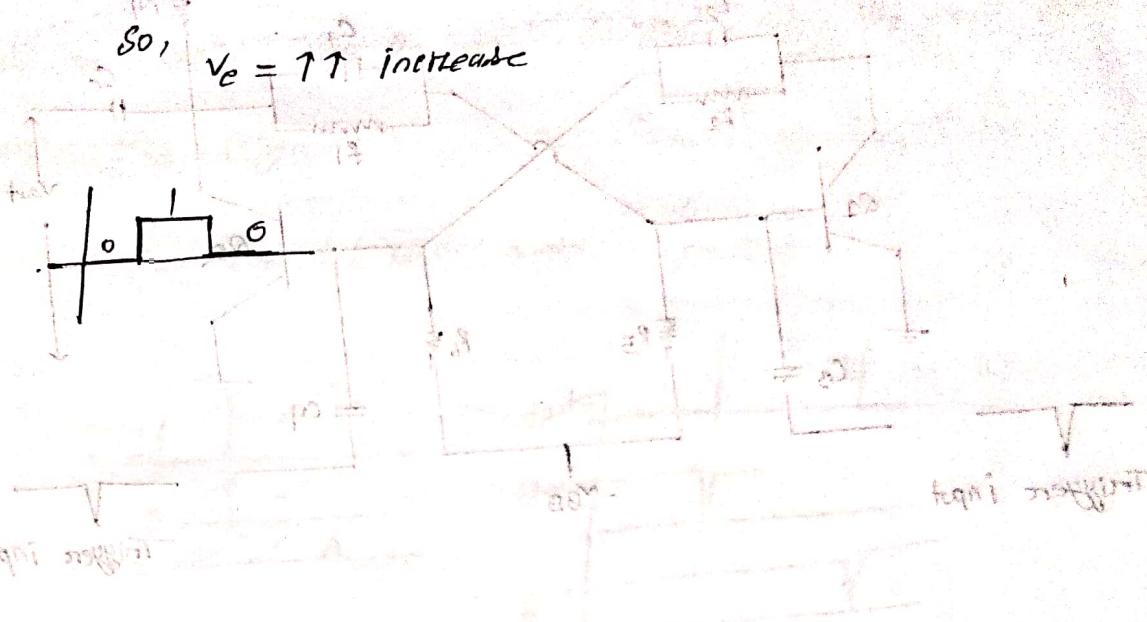

loop current analysis

(forward) current increases in one tube

current decreases in other

at one time the overall net of stage strength remains at

about 220-230


current IT = 5A

now it's only corresponds to in neglect voltage drops at

voltage No to

current IT = 5A

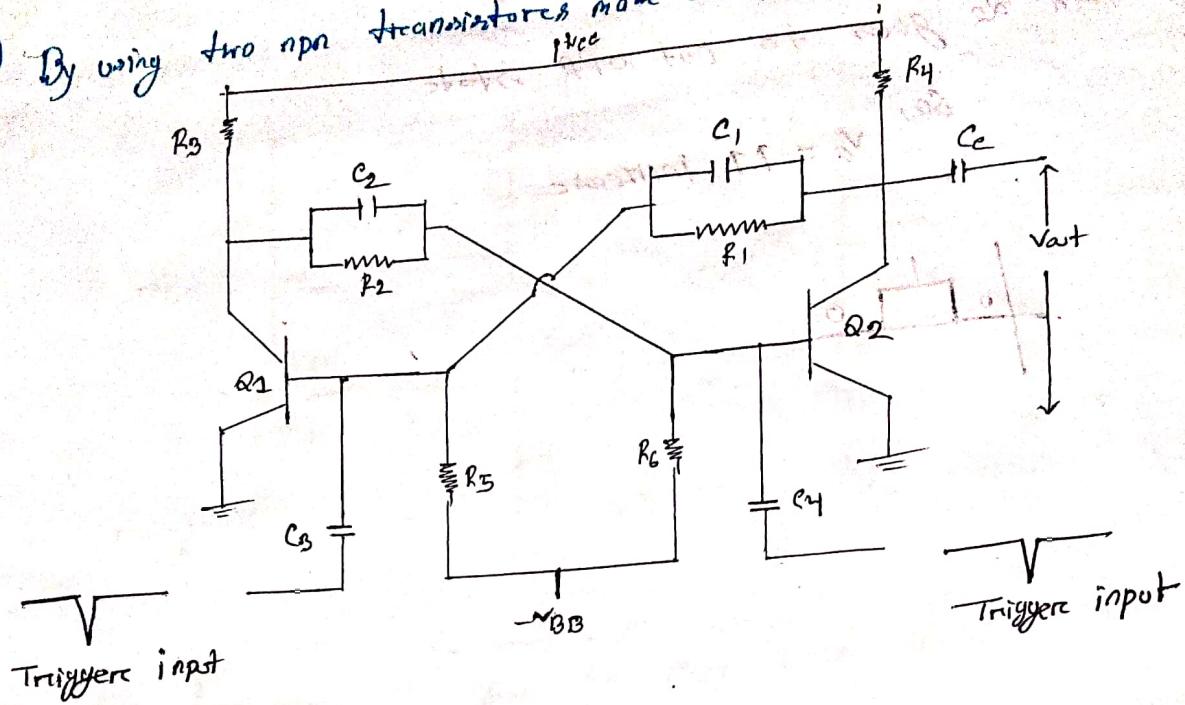Q18 By using two npn transistors make a Bi-stable Multivibrator. Explain it.



When +vee supply start then Q2 transistor start conduct,

So, $v_C = \downarrow\downarrow$ decrease

the decrease voltage v_C apply to Base Q1, So, Q1 will goes to

Cut off state,

so, $v_C = \uparrow\uparrow$ increase

when we applied negative trigger in Q2 transistor. Then Q2 go

to cut off region -



$v_C = \uparrow\uparrow$ increase.

Again Applied negative pulse trigger in α_1 , then α_1 goes to cut off state

So, $v_c = \uparrow\uparrow$ increase



The increase v_c applied in α_2 base, So, that's why α_2 more cut off to saturation region.

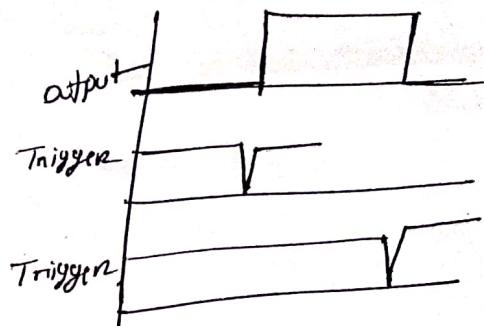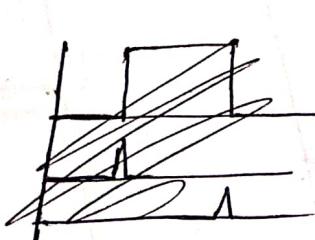So, $v_c = \downarrow\downarrow$ decrease.




Npn

Monostable

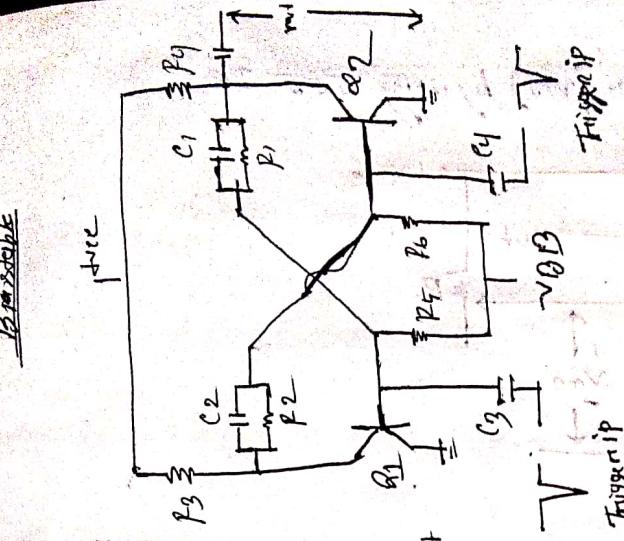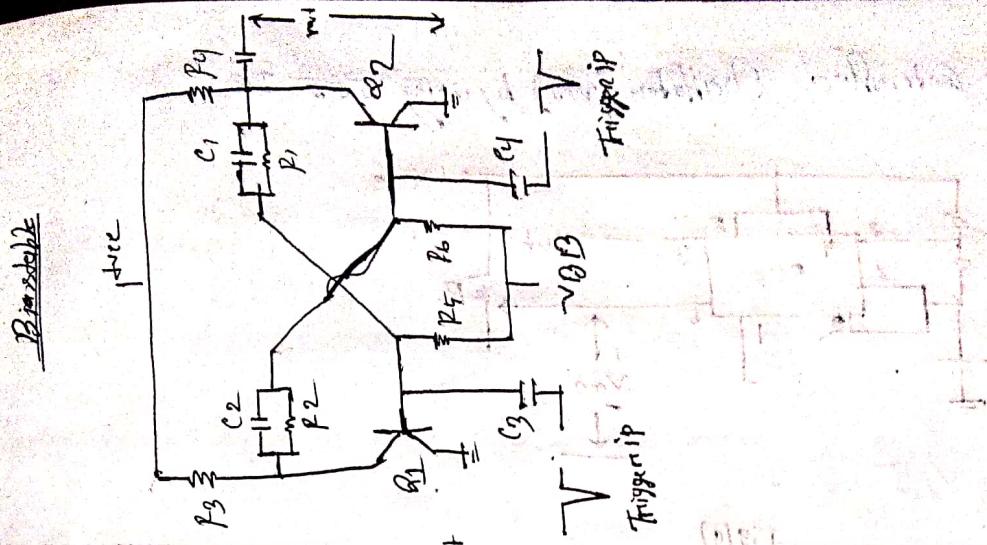


Astable

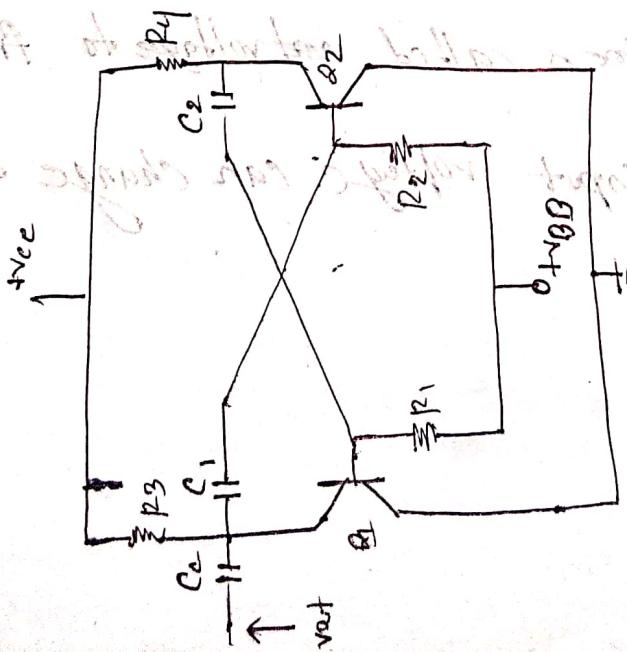


⑩ Make a voltage controlled Oscillator (VCO) by using 555 IC

Answ.

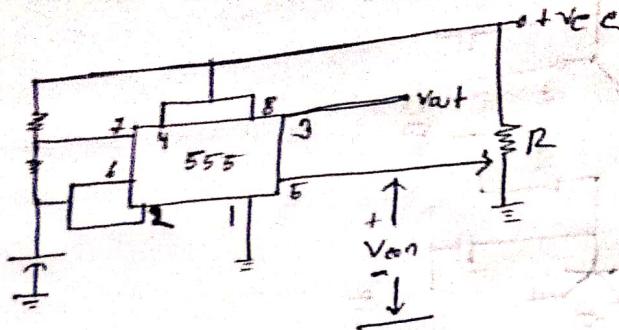

Fig(a)

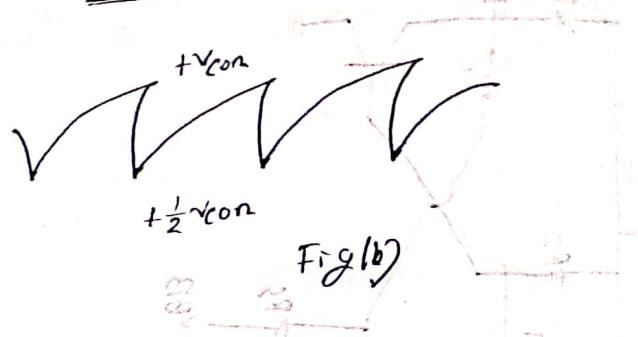


Fig(b)

Fig(a) shows a voltage controlled Oscillator (VCO) by using 555 IC.

Fig(b) shows the ~~across~~ across the timing capacitor

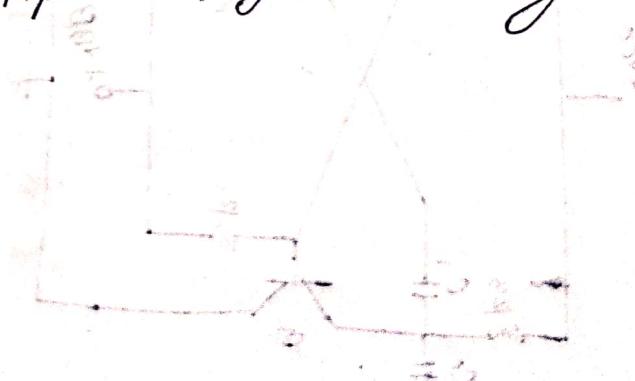This circuit is sometimes called ~~set~~ voltage to frequency converter. Because an input voltage can change output frequency.



pin-5 connect to the inverting input of the upper comparator.

normally the control voltage is $\frac{2}{3} V_{CC}$ because of the internal voltage divider.

By applying a voltage ~~in~~ in control pin, we can override the internal voltage.

if we increase $+V_{control}$ it takes the capacitor ~~longer~~ longer to

charge of discharge.

Therefore the frequency decrease.

As a result, we can change the frequency of the circuit by

varying the control voltage.

$$(S11 + S12) \left(\frac{C}{R_1} \right) + \frac{V_C}{R_2} = \frac{V_C}{R_2}$$

$$(S11 + S12) \left(\frac{C}{R_1} \right) + \frac{V_C}{R_2} = \frac{V_C}{R_2}$$

$$\left[(S11 + S12) \left(\frac{C}{R_1} \right) + \frac{V_C}{R_2} \right] \cdot \frac{300k}{3} = \frac{V_C}{R_2}$$

$$(S11 + S12) \left(\frac{C}{R_1} \right) + \frac{V_C}{R_2} = 0$$

(A) Drive diagram for calculating output frequency of oscillation.

Soln

Capacitor voltage starts at $\frac{1}{3}V_{CE}$ and ends at $\frac{2}{3}V_{CE}$
and target voltage of $V_f = V_{CE}$

$$V = V_i + (V_f - V_i) \left(1 - e^{-t/R_C}\right)$$

V = capacitor voltage

V_i = initial capacitor voltage.

V_f = target voltage.

So,

$$\frac{2}{3}V_{CE} = \frac{1}{3}V_{CE} + \left(V_{CE} - \frac{1}{3}V_{CE}\right) \left(1 - e^{-t/R_C}\right)$$

$$\Rightarrow " = " + \left(\frac{2V_{CE} - V_{CE}}{3}\right) \left(1 - e^{-t/R_C}\right)$$

$$\Rightarrow \frac{2}{3}V_{CE} = \frac{1}{3}V_{CE} + \frac{2V_{CE}}{3} \left(1 - e^{-t/R_C}\right)$$

$$\Rightarrow \frac{2}{3}V_{CE} = \frac{2V_{CE}}{3} \left[\frac{1}{2} + \left(1 - e^{-t/R_C}\right)\right]$$

$$\Rightarrow 0 = \frac{1}{2} + \left(1 - e^{-t/R_C}\right)$$

$$\Rightarrow -\frac{1}{2} = (1 - e^{-t/RC})$$

$$\Rightarrow -0.5 = 1 - \cancel{e^{-t/RC}} e^{-w/RC}$$

$$\Rightarrow -0.5 = \cancel{e^{-t/RC}} - e^{-w/RC}$$

~~$$-0.5 = \cancel{e^{-t/RC}}$$~~
$$\Rightarrow -w/RC = -0.693$$

~~$$\omega = 0.693 RC$$~~

$$\text{Charging } t_1 = (R_A + R_B) \cdot 0.693 \cancel{C}$$

$$\text{Discharging } t_2 = 0.693 R_B C$$

$$T = t_1 + t_2$$

$$= 0.693 (R_A + 2R_B) C$$

$$\text{Duty cycle: } \frac{t_1}{T} = \frac{0.693 (R_A + R_B) C}{0.693 (R_A + 2R_B) C} = \frac{R_A + R_B}{R_A + 2R_B} \times 100\%$$

$$\text{Frequency: } f = \frac{1}{T} = \frac{1}{0.693 (R_A + 2R_B) C} \text{ Ans.$$