


- ☐ Integration
- ☐ Summation
- ☒ Differentiation
- ☐ Division

Feedback

Differentiation

The following circuit is a (an) -----

3/3

 


- ☐ Inverter in CMOS
- ☐ AND gate in CMOS
- ☐ NOR gate in CMOS
- ☒ Tristate buffer in CMOS

☒ Tristate buffer in CMOS

Feedback

Tristate buffer in CMOS

 If the input is a digital pulse train, Capacitor is 1000 microFarad, Collector load is 1 K Ohm, the output of the following circuit is —



- ☐ Saw tooth wave
- ☒ Rectangular wave
- ☐ Sinusoidal wave
- ☐ exponential wave

Correct answer


- ☒ Saw tooth wave

Correct answer

- ☒ Saw tooth wave

With Enable input=1, the output of the circuit is ———

2/2

 

- ☐ Inverted
- ☐ Same as input
- ☒ Hi-Z (high impedance)

Feedback

Hi-Z (high impedance)

Which among the bipolar logic families is specifically adopted for high speed applications? 1/1


- ☐ a. Diode Transistor Logic (DTL)
- ☐ b. Transistor Transistor Logic (TTL)
- ☒ c. Emitter Coupled Logic (ECL)
- ☐ d. Integrated Injection Logic (I<sup>2</sup>L)

Feedback

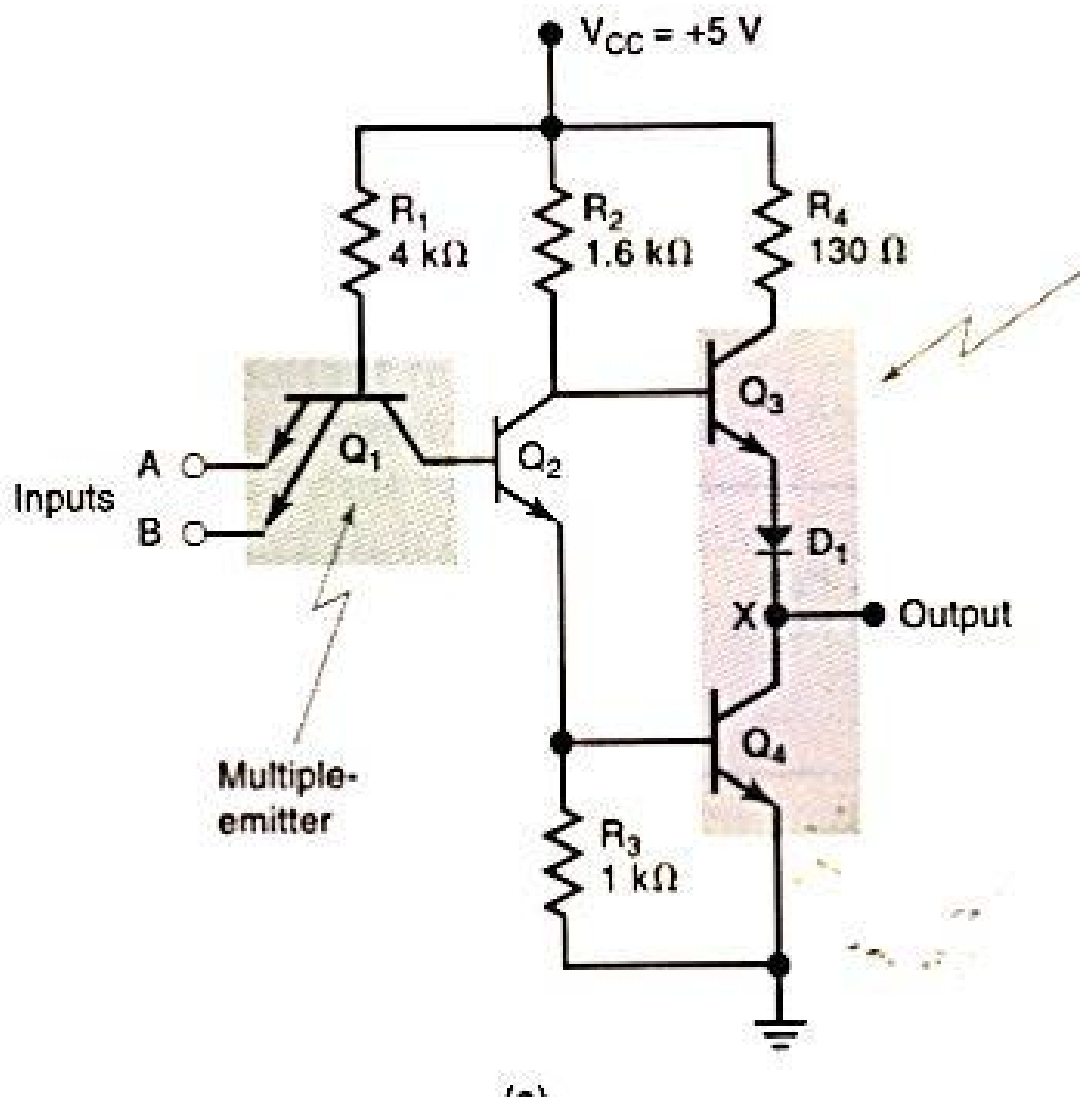c. Emitter Coupled Logic (ECL)

In the following TTL circuit, which conditions are true for the transistors Q2, Q3 and Q4 if both of the inputs A and B are set to logic zero or (A=1, B=0) or (A=0, B=1)

In the following TTL circuit, which conditions are true for the transistors Q2, Q3 and Q4 if both of the inputs A and B are set to logic zero or (A=1, B=0) or (A=0, B=1)



- ☐ Q2 ON, Q3 OFF, Q4 OFF
- ☐ Q2 OFF, Q3 OFF, Q4 ON
- ☒ Q2 OFF, Q3 ON, Q4 OFF
- ☐ Q2 ON, Q3 OFF, Q4 ON

Feedback

Q2 OFF, Q3 ON, Q4 OFF

In the following TTL circuit, which conditions are true for the transistors Q2, Q3 and Q4 if both of the inputs A and B set to logic one.

Which type of unipolar logic family exhibits its usability for the applications requiring low power consumption?

1/1

- ☐ PMOS
- ☐ NMOS
- ☒ CMOS
- ☐ All of the above

Feedback

CMOS

In the following Tri-state logic circuit, which conditions are true for the transistors T3, T4, T5 if the control input is zero.

3/3

 


Fig. 4.34

A TSL inverter.

 


Fig. 4.35


Logic symbol of a TSL inverter.

The output and input current specifications of TSL family are given in Table 4.11.

- ☐ T3 and T4 are ON but T5 is OFF
- ☒ T3, T4, T5 are OFF
- ☐ T3 is ON but T4, T5 are OFF
- ☐ T3 is OFF but T4, T5 are ON

Feedback

T3, T4, T5 are OFF

 


- ☐ Comparator
- ☒ Integrator
- ☐ Differentiator
- ☐ Summing Amplifier


Feedback

Integrator

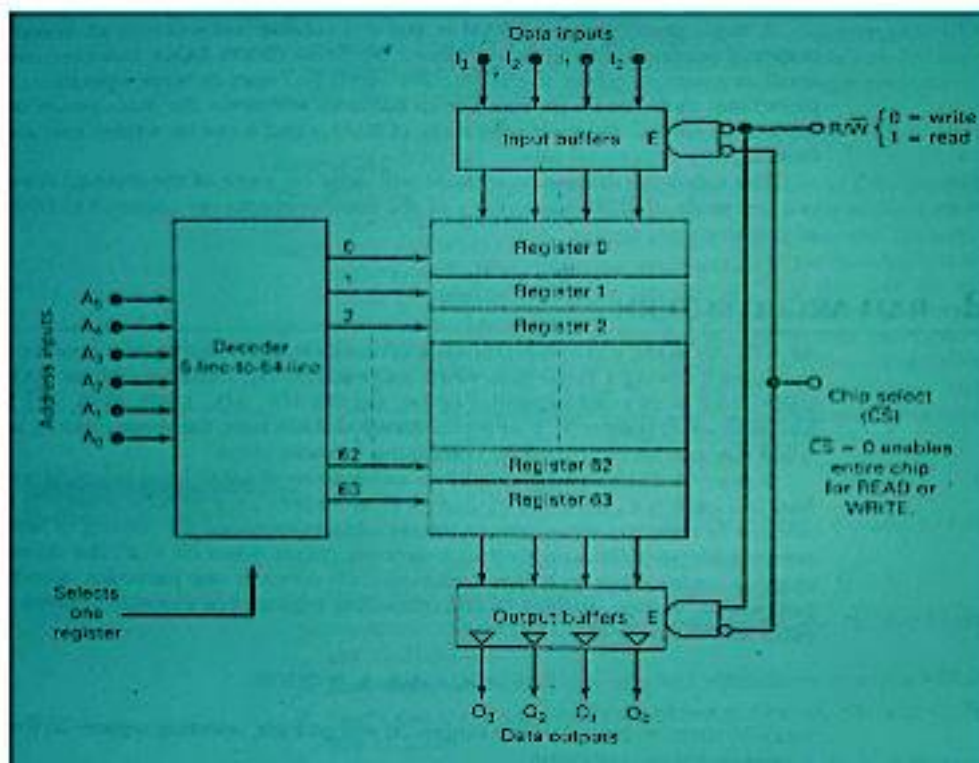Which of the following information is true for the RAM diagram given below? 2/2





 


- ☐ Its capacity is  $5 \times 64 \times 4$  bits
- ☐ Its capacity is  $6 \times 64 \times 4$  bits
- ☒ Its capacity is  $64 \times 4$  bits
- ☐ Its capacity is  $64 \times 8$  bits
- ☐ Its capacity is  $64 \times 4$  bytes

Feedback

Its capacity is  $64 \times 4$  bits

For constant voltage, the output of the circuit is ———.

2/2

 


- ☐ Time varying voltage
- ☐ Negative voltage
- ☐ Positive voltage
- ☒ Zero voltage

Feedback

Zero voltage

 If the input voltage is constant, the current through the capacitor of the circuit is 0/3 \_\_\_\_\_.



- ☐ Exponential
- ☒ Linear
- ☐ Zero
- ☐ Constant

Correct answer

- ☒ Constant

Suppose that the digital IC family has a fan out of 6. It implies that the gate can 1/1 supply the current to \_\_\_\_\_ of same family.

- ☒ 6 inputs
- ☐ 6 outputs
- ☐ 12 nodes
- ☐ 12 branches


Feedback

6 inputs



With Enable input=0, the output of the circuit is —

3/3

 



- ☐ Inverted
- ☒ Same as input
- ☐ Hi-Z (high impedance)

Feedback

Same as input

 Find the frequency of the relaxation oscillator, if  $R=1\text{ K}$ ,  $C=0.1\text{ micro Farad}$ ,  $R_1=3\text{ K}$  and  $R_2=18\text{ K}$ .



 


- ☐ 10 Hz
- ☐ 1 KHz
- ☒ 1.7 KHz
- ☐ 100 KHz

Feedback

 1.7 KHz

TTL totem pole outputs should never be tied together, because it can produce 3/3 harmful current through the transistor -----.



- ☒ Q4
- ☐ Q3
- ☐ Q1
- ☐ Q2

Feedback

Q4

In the following Tri-state logic circuit, which conditions are true for the transistors T3, T4, T5 if both of the control input and data input are set to logic one.

2/2

 


Fig. 4.34  
A TSL inverter.

 


Fig. 4.35  
Logic symbol of a TSL inverter.

The output and input current specifications of TSL family are given in Table 4.11.


- ☐ T3 and T4 are ON but T5 is OFF
- ☐ T3 is OFF but T4 and T5 are ON
- ☐ T3, T4, T5 are OFF
- ☒ T3 is ON but T4 and T5 are OFF

#### Feedback

T3 is ON but T4 and T5 are OFF

Find the voltage gain of the non-inverting amplifier.

0/2

 

-12 V

- ☐ 10
- ☐ 1
- ☐ 100
- ☒ 0.01

Correct answer

- ☒ 100

In the following Tri-state logic circuit, which conditions are true for the transistors T3, T4, T5 if the control input is logic one but data input is zero.

2/2

 


Fig. 4.34  
A TSL inverter.

 


Fig. 4.35  
Logic symbol of a TSL inverter.


The output and input current specifications of TSL family are given in Table 4.11.


- ☐ T3 and T4 are ON but T5 is OFF
- ☐ T3, T4, T5 are OFF
- ☐ T3 is ON but T4, T5 are OFF
- ☒ T3 is OFF but T4 and T5 are ON

Feedback

T3 is OFF but T4 and T5 are ON

 If the input voltage is constant, the output voltage (voltage across the capacitor) 2/2 of the circuit is -----.



 


- ☐ Exponential function of time
- ☒ Linear function of time
- ☐ Zero
- ☐ Constant

Feedback

Linear function of time

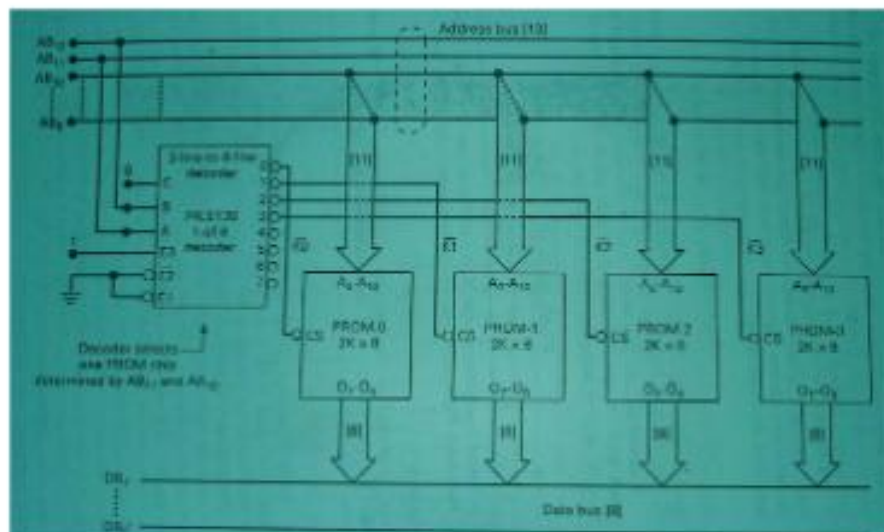There are four PROM modules in the following ROM diagram. Determine by inspection the exact address range (in hexadecimal) for the PROM-0 module. 3/3



- ☐ 0800 to 0FFF
- ☐ 1000 to 17FF
- ☐ 1800 to 1FFF
- ☒ 0000 to 07FF

Feedback

0000 to 07FF

**Feedback**

*0000 to 07FF*

Which type of output current flows towards or into the output terminal in a logic 1/1 circuit?

- ☐ Sourcing current
- ☒ Sinking current
- ☐ Both a and b
- ☐ None of the above

**Feedback**

*Sinking current*